

International University

School of Computer Science & Engineering



FINAL PROJECT

16-Bit Single Cycle Processor on FBGA

Submitted by

Truong Buu Duy – ITITIU21188

Date Submitted: 03/01/2025

Course Instructor: Dr. Vo Minh Thanh

GRADING GUIDELINE FOR LAB REPORT

Number	Content		Score	Comment
1	Format (max 9%)			
	- Font type	Yes No		
	- Font size	Yes No		
	- Lab title	Yes No		
	- Page number	Yes No		
	- Table of contents	Yes No		
	- Header/Footer	Yes No		
	- List of figures (if exists)	Yes No		
	- List of tables (if exists)	Yes No		
	- Lab report structure	Yes No		
2	English Grammar and Spelling (max 6%)			
	- Grammar	Yes No		
	- Spelling	Yes No		
3	Data and Result Analysis (max 85%)			
Total Score				

Signature:

Date:

TABLE OF CONTENTS

1	THEORETICAL BACKGROUND	1
1.1	Program Counter	1
1.2	ADD	1
1.3	Instruction Memory	1
1.4	ALU	2
1.5	Mux	3
1.6	Sign Extend	3
1.7	Register File	3
1.8	Data Memory	4
1.9	Instructions	4
2	EXPERIMENTAL PROCEDURE AND RESULTS	6
2.1	Data Memory	6
2.2	Instruction Memory	9
2.3	Program Counter	14
2.4	Register File	17
2.5	Adder 32 Bit	21
2.6	Mux N bit	23
2.7	Sign Extend N bit to 32 bit	25
2.8	ALU 16 Bits	27
2.9	Completed Processor	31

LIST OF FIGURES

<i>Figure 1.1 Program Counter Module</i>	<i>1</i>
<i>Figure 1.2 ADD Module</i>	<i>1</i>
<i>Figure 1.3 Instruction Memory Module</i>	<i>2</i>
<i>Figure 1.4 ALU Module</i>	<i>2</i>
<i>Figure 1.5 Mux Module</i>	<i>3</i>
<i>Figure 1.6 Sign Extend Module</i>	<i>3</i>
<i>Figure 1.7 Register File Module</i>	<i>4</i>
<i>Figure 1.8 Data Memory Module</i>	<i>4</i>
<i>Figure 2.1 Single Cycle Microprocessor Schematic</i>	<i>31</i>

LIST OF TABLES

<i>Table 1.1 R-Type Instructions</i>	<hr/>	<i>4</i>
<i>Table 1.2 I-Type Instructions</i>	<hr/>	<i>5</i>
<i>Table 1.3 J-Type Instructions</i>	<hr/>	<i>5</i>

NOMENCLATURE

PC	Program Counter
ALU	Algorithm Logic Uni
Mux	Multiplexer
Clk	Clock

1 THEORETICAL BACKGROUND

1.1 Program Counter

This module's purpose is to determine whether the cycle operates using a new input signal or resets the system input to 0.

 


Figure 1.1 Program Counter Module

1.2 ADD

This module is used to sum up 2 input signals which have the same number of bits.

 


Figure 1.2 ADD Module

1.3 Instruction Memory

This module provides instructions to other components based on the input signal. The system generates a 5-bit signal for the memory register and controller and a 16-bit signal for the adder ALU operator. Instructions indexed 0-5 are sent to the ALU operator controller, while instructions indexed 0-15 pass through a signal extender to the ALU adder. Instructions indexed 16-20 pass

through a MUX with indices 11-15 before reaching Read Register 2. Instructions indexed 21-25 are directed to Read Register 1.

 


Figure 1.3 Instruction Memory Module

1.4 ALU

This module receives the operating instruction from operator wire and 2 input signals as parameters. Output of this module is the result of the operation.

 


Figure 1.4 ALU Module

1.5 Mux

This module is to choose the output signal, which is one of the input signals.

 


Figure 1.5 Mux Module

1.6 Sign Extend

To convert from 16 bits signal to 32 bits signal, we use signal extender. The extending bits equal the highest bit of the 16 bits signal.

 


Figure 1.6 Sign Extend Module

1.7 Register File

This module has to role of operating to data memory. The receive instruction would come in from the RN1, RN2 and WN port with 5 bits signals. RegWrite to enable writing data 32 bits signal received 32 bits signal from WD port into a specific address provided by WN.

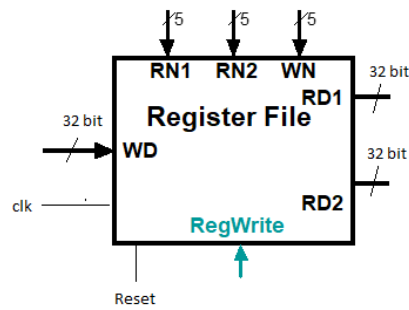


Figure 1.7 Register File Module

1.8 Data Memory

The operator is used to access memory data with the granted address of ADDR port. MemWrite and MemRead would enable/disable reading and writing process of Memory data. At the given address, the data may be export through RD and replace with the input data from WD.

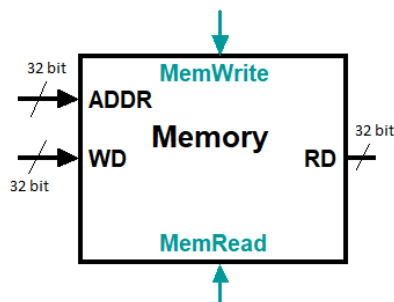


Figure 1.8 Data Memory Module

1.9 Instructions

Table 1.1 R-Type Instructions

Instruction	Operation	Function
add rd,rs,rt	$rd = rs + rt$	100000
sub rd,rs,rt	$rd = rs - rt$	100010
and rd,rs,rt	$rd = rs \& rt$	100100

or rd,rs,rt	$rd = rs \mid rt$	100101
nor rd,rs,rt	$rd = \sim(rs \mid rt)$	100111
xor rd,rs,rt	$rd = rs \wedge rt$	100110
nand rd,rs,rt	$rd = \sim(rs \& rt)$	101000
xnor rd,rs,rt	$rd = \sim(rs \wedge rt)$	101010
sll rd,rt,shamt	$rd = rt \ll shamt$	000000
srl rd,rt,shamt	$rd = rt \gg shamt$	000010
ror rd,rt,rs	$rd = (rt \gg shamt) \mid (rt \ll (32 - shamt))$	110000
rol rd,rt,rs	$rd = (rt \ll shamt) \mid (rt \gg (32 - shamt))$	111000

Table 1.2 I-Type Instructions

Instruction	Operation	Opcode
addi rt,rs,imm	$rt = rs + imm$	001000
beq rs,rt,imm	if $(rs == rt)$ then branch	000100
bne rs,rt,imm	if $!(rs == rt)$ then branch	000101
lw rt,offset(rs)	$rt = mem[offset + rs]$	100011
sw rt,offset(rs)	$mem[offset + rs] = rt$	101011

Table 1.3 J-Type Instructions

Instruction	Operation	Opcode
j address	jump to the instruction with respect address	000010
jal target	jump to the instruction at the specified address and save the return address in the \$ra (register 31), which allows returning to the next instruction after the jump.	000011

2 EXPERIMENTAL PROCEDURE AND RESULTS

2.1 Data Memory

Verilog code
<pre>//Data Memory 16 bit module Data_Memory_16bit (clk,addr,write_data,read_data,MemRead,MemWrite); input clk; input [15:0] addr; input [15:0] write_data; output reg [15:0] read_data; input MemRead; input MemWrite; integer i; reg [15:0] DMemory [0:255]; initial begin for (i = 0; i < 256; i = i + 1) begin DMemory[i] = 16'h0000; end end always @(posedge clk) begin if (MemWrite) begin DMemory[addr] <= write_data; \$display("Memory Write: Address=%h Data=%h", addr, write_data); end end always @(*) begin if (MemRead) read_data = DMemory[addr]; end end</pre>

```

        else
            read_data = 16'h0000;
        end
    endmodule

```

Testbench

```

// Testbench
module tb_Data_Memory_16bit;

    reg clk,MemRead,MemWrite;
    reg [15:0] addr,write_data;

    wire [15:0] read_data;

    Data_Memory_16bit
    uut(.clk(clk),.addr(addr),.write_data(write_data),.read_data(read_data),.MemRead(MemRead)
    ,.MemWrite(MemWrite));

    always #5 clk = ~clk;

    initial begin
        clk = 0;
        addr = 16'h0000;
        write_data = 16'h0000;
        MemRead = 0;
        MemWrite = 0;

        $display("\n-----Test Data Memory 16 bit-----");

        $monitor("Time=%0t | Addr=%h | WriteData=%h | ReadData=%h | MemRead=%b |
        MemWrite=%b",
            $time, addr, write_data, read_data, MemRead, MemWrite);
    end

```

```
// Write data to memory
#10;
addr = 16'h0001;
write_data = 16'h1234;
MemWrite = 1;
MemRead = 0;
#10;
MemWrite = 0; // Stop write

// Read data from memory
#10;
addr = 16'h0001;
MemRead = 1;
#10;
MemRead = 0; // Stop read

// Write
#10;
addr = 16'h0002;
write_data = 16'h5678;
MemWrite = 1;
#10;
MemWrite = 0;

// Read
#10;
addr = 16'h0002;
MemRead = 1;
#10;
MemRead = 0;
```

<pre> // Test reading an uninitialized memory location #10; addr = 16'h00FF; MemRead = 1; #10; MemRead = 0; #20; \$finish; end endmodule </pre>	
Result	
<pre> -----Test Data Memory 16 bit----- Time=0 Addr=0000 WriteData=0000 ReadData=0000 MemRead=0 MemWrite=0 Time=10 Addr=0001 WriteData=1234 ReadData=0000 MemRead=0 MemWrite=1 Memory Write: Address=0001 Data=1234 Time=20 Addr=0001 WriteData=1234 ReadData=0000 MemRead=0 MemWrite=0 Time=30 Addr=0001 WriteData=1234 ReadData=1234 MemRead=1 MemWrite=0 Time=40 Addr=0001 WriteData=1234 ReadData=0000 MemRead=0 MemWrite=0 Time=50 Addr=0002 WriteData=5678 ReadData=0000 MemRead=0 MemWrite=1 Memory Write: Address=0002 Data=5678 Time=60 Addr=0002 WriteData=5678 ReadData=0000 MemRead=0 MemWrite=0 Time=70 Addr=0002 WriteData=5678 ReadData=5678 MemRead=1 MemWrite=0 Time=80 Addr=0002 WriteData=5678 ReadData=0000 MemRead=0 MemWrite=0 Time=90 Addr=00ff WriteData=5678 ReadData=0000 MemRead=1 MemWrite=0 Time=100 Addr=00ff WriteData=5678 ReadData=0000 MemRead=0 MemWrite=0 jdoodle.v:65: \$finish called at 120 (1s) </pre>	

2.2 Instruction Memory

Verilog code
// Instruction Memory

```

module Instruction_Memory (read_address, instruction, reset);

    input reset;
    input [31:0] read_address;
    output [31:0] instruction;
    reg [31:0] Imemory [256:0];
    integer i;
    assign instruction = Imemory[read_address];
    always @(posedge reset)
    begin
        for (i=0; i<32; i=i+1)
            begin
                Imemory[i] = 32'b0;
            end
        /*Test R-type*/
        // add $s6, $s5, $s4      R22 = R21 + R20 = 0x7 (0x5 + 0x2)
        Imemory[0] = 32'b000000_10101_10100_10110_00000_100000;
        // sub $s6, $s5, $s4      R22 = R21 - R20 = 0x3 (0x5 - 0x2)
        Imemory[1] = 32'b000000_10101_10100_10110_00000_100010;
        // mult $s5, $s4          R21 * R20 = 0xA (0x5 * 0x2)
        Imemory[2] = 32'b000000_10101_10100_00000_00000_011000;
        // div $s5, $s4          R21 / R20 = 0x2 (0x5 / 0x2)
        Imemory[3] = 32'b000000_10101_10100_00000_00000_011010;
        // and $s6, $s5, $s4      R22 = AND(R21, R20) = 0x0 (0x5 AND 0x2)
        Imemory[4] = 32'b000000_10101_10100_10110_00000_100100;
        // or $s6, $s5, $s4       R22 = OR(R21, R20) = 0x7 (0x5 OR 0x2)
        Imemory[5] = 32'b000000_10101_10100_10110_00000_100101;
        // xor $s6, $s5, $s4      R22 = XOR(R21, R20) = 0x7 (0x5 XOR 0x2)
        Imemory[6] = 32'b000000_10101_10100_10110_00000_100110;
        // nor $s6, $s5, $s4      R22 = NOR(R21, R20) = 0xFFFFFFF8 (NOR of 0x5
and 0x2)
        Imemory[7] = 32'b000000_10101_10100_10110_00000_100111;
    end
end

```



```

// nand $s6, $s5, $s4      R22 = NAND(R21, R20) = 0xFFFFFFFFD (NAND of
0x5 and 0x2)

Imemory[8] = 32'b000000_10101_10100_10110_00000_101000;
// xnor $s6, $s5, $s4      R22 = XNOR(R21, R20) = 0xFFFFFFFFE (XNOR of
0x5 and 0x2)

Imemory[9] = 32'b000000_10101_10100_10110_00000_101010;
// sll $s6, $s5, $s4      R22 = R21 << R20 = 0x14 (0x5 << 0x2)
Imemory[10] = 32'b000000_10101_10100_10110_00000_000000;
// srl $s6, $s5, $s4      R22 = R21 >> R20 = 0x1 (0x5 >> 0x2)
Imemory[11] = 32'b000000_10101_10100_10110_00000_000010;
// rol $s6, $s5           R22 = R21 rotated 1 bit left = 0xA (rotate 0x5 left by 1)
Imemory[12] = 32'b000000_10101_00000_10110_00000_111000;
// ror $s6, $s5           R22 = R21 rotated 1 bit right = 0x2 (rotate 0x5 right by
1)

Imemory[13] = 32'b000000_10101_00000_10110_00000_110000;

/*Test I-type*/
// addi $s1, $s1, 0x05     R17 = 0x4E => R17 = R17 + 0x5 = 0x53
Imemory[14] = 32'b001000_10001_10001_00000_00000_000101;
// addi $s1, $s1, 0x05     R17 = 0x53 => R17 = R17 + 0x5 = 0x58
Imemory[15] = 32'b001000_10001_10001_00000_00000_000101;
// addi $s3, $s1, 0x10     R17 = 0x58 => R19 = R17 + 0x10 = 0x68
Imemory[16] = 32'b001000_10001_10011_00000_00000_010000;
// sw $s3, 0x04($s1)      Memory[$s1 + 0x04] = $s3 => Memory[0x58 + 0x04] = 0x68
Imemory[17] = 32'b101011_10001_10011_00000_00000_000100;
// lw $s7, 0x04($s1)      $s7 = Memory[$s1 + 0x04] = 0x68
Imemory[18] = 32'b100011_10001_10111_00000_00000_000100;
// beq $s7, $s3, 0x08     R23 (0x68) == R19 (0x68) move to Imemory[22 + 8 + 1]
Imemory[19] = 32'b000100_10111_10011_00000_00000_001000;
// addi $s1, $zero, 0x11   R17 = 0x11
Imemory[20] = 32'b001000_00000_10001_00000_00000_010001;

```

```

// addi $s1, $zero, 0x22    R17 = 0x22
Imemory[21] = 32'b001000_00000_10001_00000_00000_100010;
// addi $s1, $zero, 0x33    R17 = 0x33
Imemory[22] = 32'b001000_00000_10001_00000_00000_110011;
// bne $s1, $s7, 0x04      (R17 (0x33) != R23 (0x68)) move to Imemory[26 + 4 + 1]
Imemory[23] = 32'b000101_10001_10111_00000_00000_000100;
// addi $s2, $zero, 0x66    R18 = 0x66
Imemory[24] = 32'b001000_00000_10010_00000_00001_100110;
// addi $s2, $zero, 0x77    R18 = 0x77
Imemory[25] = 32'b001000_00000_10010_00000_00001_110111;

/* Test J-type */
    // j 0x74 (JUMP to Imemory[116])
    Imemory[26] = 32'b000010_00000_00000_00000_00001_110100;
    // jal 0x74 (Jump and Link to Imemory[116])
    Imemory[27] = 32'b000011_00000_00000_00000_00001_110100;
    // j 0x78 (JUMP to Imemory[120])
    Imemory[28] = 32'b000010_00000_00000_00000_00001_111000;
    // jal 0x78 (Jump and Link to Imemory[120])
    Imemory[29] = 32'b000011_00000_00000_00000_00001_111000;
    // j 0x64 (JUMP to Imemory[100])
    Imemory[30] = 32'b000010_00000_00000_00000_00001_100100;
    // jal 0x68 (Jump and Link to Imemory[104])
    Imemory[31] = 32'b000011_00000_00000_00000_00001_101000;
    // j 0x6C (JUMP to Imemory[108])
    Imemory[32] = 32'b000010_00000_00000_00000_00001_101100;
    // jal 0x70 (Jump and Link to Imemory[112])
    Imemory[33] = 32'b000011_00000_00000_00000_00001_110000;
    // j 0x74 (JUMP to Imemory[116])
    Imemory[34] = 32'b000010_00000_00000_00000_00001_110100;
    // j 0x7C (JUMP to Imemory[124])

```

```

        Imemory[35] = 32'b000010_00000_00000_00000_00001_111100;

    end
endmodule

```

Testbench
<pre> // Testbench module tb_Instruction_Memory; reg reset; reg [31:0] read_address; wire [31:0] instruction; Instruction_Memory uut(.reset(reset),.read_address(read_address),.instruction(instruction)); initial begin \$display("\n-----Test Instruction Memory-----"); \$monitor("Time=%0d reset=%b read_address=%2d instruction=%h", \$time, reset, read_address, instruction); reset = 0; read_address = 32'd0; // Test Case 1 #5 reset = 1; #10 reset = 0; // Test Case 2 #10 read_address = 32'd0; // Address 0 #10 read_address = 32'd0; // Address 0 #10 read_address = 32'd1; // Address 1 </pre>

<pre> #10 read_address = 32'd10; // Address 10 #10 read_address = 32'd3; // Address 3 #10 read_address = 32'd4; // Address 4 #10 read_address = 32'd16; // Address 16 #10 read_address = 32'd6; // Address 6 #10 read_address = 32'd7; // Address 7 #10 read_address = 32'd29; // Address 29 #50 \$finish; end endmodule </pre>
Result
<pre> -----Test Instruction Memory----- Time=0 reset=0 read_address= 0 instruction=xxxxxxx Time=5 reset=1 read_address= 0 instruction=02b4b020 Time=15 reset=0 read_address= 0 instruction=02b4b020 Time=45 reset=0 read_address= 1 instruction=02b4b022 Time=55 reset=0 read_address=10 instruction=02b4b000 Time=65 reset=0 read_address= 3 instruction=02b4001a Time=75 reset=0 read_address= 4 instruction=02b4b024 Time=85 reset=0 read_address=16 instruction=22330010 Time=95 reset=0 read_address= 6 instruction=02b4b026 Time=105 reset=0 read_address= 7 instruction=02b4b027 Time=115 reset=0 read_address=29 instruction=0c000078 jdoodle.v:35: \$finish called at 165 (1s) </pre>

2.3 Program Counter

Verilog code
<pre>// Program Counter</pre>

```
module Program_Counter(clk, reset, PC_in, PC_out);
```

```
    input clk, reset;
```

```
    input [31:0] PC_in;
```

```
    output reg [31:0] PC_out;
```

```
    always @(posedge clk) begin
```

```
        if(reset)
```

```
            PC_out <= 32'b0;
```

```
        else
```

```
            PC_out <= PC_in;
```

```
    end
```

```
endmodule
```

Testbench

```
// Testbench
```

```
module tb_Program_Counter;
```

```
    reg clk, reset;
```

```
    reg [31:0] PC_in;
```

```
    wire [31:0] PC_out;
```

```
    Program_Counter uut(.clk(clk),.reset(reset),.PC_in(PC_in),.PC_out(PC_out));
```

```
    always #5 clk = ~clk;
```

```
    initial begin
```

```
        clk = 0;
```

```
        reset = 1;
```

```
        PC_in = 32'd0;
```

```
        $display("\n-----Test Program Counter 32 bit-----");
```

```
        $monitor("Time=%0t|reset=%b | clk=%b | PC_in=%h | PC_out=%h |", $time,reset, clk,
```

```
PC_in, PC_out);
```

```
    #10 reset = 0;
```

```
    repeat(10) begin
```

```
        #10 PC_in = $random;
```

```
    end
```

```
    #10 reset = 1;
```

```
    #10 reset = 0;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Result

-----Test Program Counter 32 bit-----

Time=0	reset=1	clk=0	PC_in=00000000	PC_out=xxxxxxxx
Time=5	reset=1	clk=1	PC_in=00000000	PC_out=00000000
Time=10	reset=0	clk=0	PC_in=00000000	PC_out=00000000
Time=15	reset=0	clk=1	PC_in=00000000	PC_out=00000000
Time=20	reset=0	clk=0	PC_in=12153524	PC_out=00000000
Time=25	reset=0	clk=1	PC_in=12153524	PC_out=12153524
Time=30	reset=0	clk=0	PC_in=c0895e81	PC_out=12153524
Time=35	reset=0	clk=1	PC_in=c0895e81	PC_out=c0895e81
Time=40	reset=0	clk=0	PC_in=8484d609	PC_out=c0895e81
Time=45	reset=0	clk=1	PC_in=8484d609	PC_out=8484d609
Time=50	reset=0	clk=0	PC_in=b1f05663	PC_out=8484d609
Time=55	reset=0	clk=1	PC_in=b1f05663	PC_out=b1f05663
Time=60	reset=0	clk=0	PC_in=06b97b0d	PC_out=b1f05663
Time=65	reset=0	clk=1	PC_in=06b97b0d	PC_out=06b97b0d
Time=70	reset=0	clk=0	PC_in=46df998d	PC_out=06b97b0d
Time=75	reset=0	clk=1	PC_in=46df998d	PC_out=46df998d
Time=80	reset=0	clk=0	PC_in=b2c28465	PC_out=46df998d
Time=85	reset=0	clk=1	PC_in=b2c28465	PC_out=b2c28465
Time=90	reset=0	clk=0	PC_in=89375212	PC_out=b2c28465
Time=95	reset=0	clk=1	PC_in=89375212	PC_out=89375212
Time=100	reset=0	clk=0	PC_in=00f3e301	PC_out=89375212
Time=105	reset=0	clk=1	PC_in=00f3e301	PC_out=00f3e301
Time=110	reset=0	clk=0	PC_in=06d7cd0d	PC_out=00f3e301
Time=115	reset=0	clk=1	PC_in=06d7cd0d	PC_out=06d7cd0d
Time=120	reset=1	clk=0	PC_in=06d7cd0d	PC_out=06d7cd0d
Time=125	reset=1	clk=1	PC_in=06d7cd0d	PC_out=00000000
jdoodle.v:29: \$finish called at 130 (1s)				
Time=130	reset=0	clk=0	PC_in=06d7cd0d	PC_out=00000000

2.4 Register File

Verilog code

```
// Register File 16bit
module Register_File_16bit (clk,read_addr_1, read_addr_2, write_addr, write_data,
RegWrite,read_data_1, read_data_2);
    input clk,RegWrite;
    input [4:0] read_addr_1, read_addr_2, write_addr;
    input [15:0] write_data;
    output [15:0] read_data_1, read_data_2;
    reg [15:0] Regfile [31:0];
    integer i;

    initial begin
        for (i = 0; i < 32; i = i + 1) begin
            Regfile[i] = 16'b0;
        end
        Regfile[19]=1; // $s3 = 1
        Regfile[17]=3; // $s1 = 3
        Regfile[20]=2; // $s4 = 2
        Regfile[21]=5; // $s5 = 5
    end

    assign read_data_1 = Regfile[read_addr_1];
    assign read_data_2 = Regfile[read_addr_2];

    always @(posedge clk) begin
        if (RegWrite) begin
            Regfile[write_addr] <= write_data;
            $display("write_addr=%h write_data=%h",write_addr,write_data);
        end
    end
endmodule
```


Testbench

```
// Testbench
module tb_Register_File_16bit;
    reg clk,RegWrite;
    reg [4:0] read_addr_1, read_addr_2, write_addr;
    reg [15:0] write_data;
    wire [15:0] read_data_1, read_data_2;

    Register_File_16bit uut
    (.clk(clk),.read_addr_1(read_addr_1),.read_addr_2(read_addr_2),.write_addr(write_addr),.write_data(write_data),.RegWrite(RegWrite),.read_data_1(read_data_1),.read_data_2(read_data_2));

    always #5 clk = ~clk;

    initial begin
        clk = 0;
        RegWrite = 0;
        read_addr_1 = 5'b0;
        read_addr_2 = 5'b0;
        write_addr = 5'b0;
        write_data = 16'b0;

        $display("\n-----Test Register File 16 bit-----");

        $monitor("Time=%0t    |   ReadAddr1=%h   ReadData1=%h    |   ReadAddr2=%h   ReadData2=%h | WriteAddr=%h WriteData=%h RegWrite=%b",
            $time, read_addr_1, read_data_1, read_addr_2, read_data_2, write_addr, write_data, RegWrite);
    end
endmodule
```

```

// Read default values from registers
#10;
read_addr_1 = 5'd19; // Reading $s3
read_addr_2 = 5'd17; // Reading $s1

#10;
read_addr_1 = 5'd20; // Reading $s4
read_addr_2 = 5'd21; // Reading $s5

// Write to a register
#10;
write_addr = 5'd10; // Write to $t2
write_data = 16'h1234;
RegWrite = 1;
#10;
RegWrite = 0;

// Read back the written value
#10;
read_addr_1 = 5'd10; // Reading $t2
read_addr_2 = 5'd20; // Reading $s4

// Write to another register
#10;
write_addr = 5'd5; // Write to $a1
write_data = 16'h5678;
RegWrite = 1;
#10;
RegWrite = 0;

```

<pre> // Read back the new values #10; read_addr_1 = 5'd5; // Reading \$a1 read_addr_2 = 5'd10; // Reading \$t2 #20; \$finish; end endmodule </pre>	
Result	
<pre> -----Test Register File 16 bit----- Time=0 ReadAddr1=00 ReadData1=0000 ReadAddr2=00 ReadData2=0000 WriteAddr=00 WriteData=0000 RegWrite=0 Time=10 ReadAddr1=13 ReadData1=0001 ReadAddr2=11 ReadData2=0003 WriteAddr=00 WriteData=0000 RegWrite=0 Time=20 ReadAddr1=14 ReadData1=0002 ReadAddr2=15 ReadData2=0005 WriteAddr=00 WriteData=0000 RegWrite=0 Time=30 ReadAddr1=14 ReadData1=0002 ReadAddr2=15 ReadData2=0005 WriteAddr=0a WriteData=1234 RegWrite=1 write_addr=0a write_data=1234 Time=40 ReadAddr1=14 ReadData1=0002 ReadAddr2=15 ReadData2=0005 WriteAddr=0a WriteData=1234 RegWrite=0 Time=50 ReadAddr1=0a ReadData1=1234 ReadAddr2=14 ReadData2=0002 WriteAddr=0a WriteData=1234 RegWrite=0 Time=60 ReadAddr1=0a ReadData1=1234 ReadAddr2=14 ReadData2=0002 WriteAddr=05 WriteData=5678 RegWrite=1 write_addr=05 write_data=5678 Time=70 ReadAddr1=0a ReadData1=1234 ReadAddr2=14 ReadData2=0002 WriteAddr=05 WriteData=5678 RegWrite=0 Time=80 ReadAddr1=05 ReadData1=5678 ReadAddr2=0a ReadData2=1234 WriteAddr=05 WriteData=5678 RegWrite=0 jdoodle.v:63: \$finish called at 100 (1s) </pre>	

2.5 Adder 32 Bit

Verilog code
<pre> // Adder 32 bit module Adder32Bit(input1, input2, out); input [31:0] input1, input2; output [31:0] out; reg [31:0]out; always@(input1 or input2) begin </pre>

```

        out <= input1 + input2;
    end
endmodule

```

Testbench

```

module tb_Adder32Bit;

    reg signed [31:0] input1, input2;
    wire [31:0] out;

    Adder32Bit uut (.input1(input1),.input2(input2),.out(out));

    initial begin
        $display("-----Test Adder 32 bit-----");

        $monitor("Time=%0t | input1 = %d | input2 = %d | out = %d", $time, input1, input2, out);

        // Test case 1: Add two positive numbers
        input1 = 32'd25;
        input2 = 32'd30;
        #10;
        // Test case 2: Add a positive and a negative number
        input1 = 32'd100;
        input2 = -32'd50;
        #10;
        // Test case 3: Add two large numbers
        input1 = 32'd4294967295; // Max unsigned 32-bit value
        input2 = 32'd1;
        #10;

        $finish;
    end
endmodule

```

endmodule

Result

-----Test Adder 32 bit-----

```
Time=0 | input1 =      25 | input2 =      30 | out =      55
Time=10 | input1 =     100 | input2 =     -50 | out =      50
Time=20 | input1 =      -1 | input2 =       1 | out =       0
jdoodle.v:35: $finish called at 30 (1s)
```

2.6 Mux N bit

Verilog code

```
// Mux N bit
module Mux_N_bit (in0, in1, mux_out, select);
    parameter N=5;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select ? in1 : in0;
endmodule
```

Testbench

```
// Testbench
module tb_Mux_N_bit;
    reg [4:0] in0_5, in1_5;
    reg [15:0] in0_16, in1_16;
    reg [31:0] in0_32, in1_32;
    wire [4:0] mux_out_5;
    wire [15:0] mux_out_16;
    wire [31:0] mux_out_32;
    reg select;
```

```

Mux_N_bit #(5) uut_5 (.in0(in0_5), .in1(in1_5), .mux_out(mux_out_5), .select(select));
Mux_N_bit  #(16)  uut_16  (.in0(in0_16),  .in1(in1_16),  .mux_out(mux_out_16),
.select(select));
Mux_N_bit  #(32)  uut_32  (.in0(in0_32),  .in1(in1_32),  .mux_out(mux_out_32),
.select(select));

initial begin
    select = 0;
    in0_5 = 5'b00001; in1_5 = 5'b00010;
    in0_16 = 16'h1234; in1_16 = 16'h5678;
    in0_32 = 32'hABCDEF12; in1_32 = 32'h98765432;

    $display("-----Test Mux N bit-----");
    $monitor("Time=%0t Select=%b \n\tN=5  : in0=%b| in1=%b| mux_out=%b \n\tN=16:
in0=%h| in1=%h| mux_out=%h \n\tN=32: in0=%h| in1=%h| mux_out=%h",
        $time, select, in0_5, in1_5, mux_out_5, in0_16, in1_16, mux_out_16, in0_32, in1_32,
mux_out_32);

    #1;

    #10;
    select = 0;
    in0_5 = 5'b10101; in1_5 = 5'b11011;
    in0_16 = 16'hA5A5; in1_16 = 16'h5A5A;
    in0_32 = 32'h12345678; in1_32 = 32'h87654321;

    #10;
    select = 1;
    in0_5 = 5'b01010; in1_5 = 5'b11111;
    in0_16 = 16'hABCD; in1_16 = 16'hDCBA;
    in0_32 = 32'h1A2B3C4D; in1_32 = 32'h4D3C2B1A;

```

```

    #10;
    $finish;
end
endmodule

```

Result

```

-----Test Mux N bit-----
Time=0 Select=0
  N=5  : in0=00001| in1=00010| mux_out=00001
  N=16: in0=1234| in1=5678| mux_out=1234
  N=32: in0=abcdef12| in1=98765432| mux_out=abcdef12
Time=11 Select=0
  N=5  : in0=10101| in1=11011| mux_out=10101
  N=16: in0=a5a5| in1=5a5a| mux_out=a5a5
  N=32: in0=12345678| in1=87654321| mux_out=12345678
Time=21 Select=1
  N=5  : in0=01010| in1=11111| mux_out=11111
  N=16: in0=abcd| in1=dcba| mux_out=dcba
  N=32: in0=1a2b3c4d| in1=4d3c2b1a| mux_out=4d3c2b1a
jdoodle.v:40: $finish called at 31 (1s)

```

2.7 Sign Extend N bit to 32 bit

Verilog code

```

// Sign Extension N-bit
module Sign_Extension_N_bit (sign_in, sign_out);
    parameter N = 16;
    input [N-1:0] sign_in;
    output [31:0] sign_out;

    assign sign_out = {{(32-N){sign_in[N-1]}}, sign_in};

```

endmodule

Testbench

// Testbench

module tb_Sign_Extension_N_bit;

reg [15:0] sign_in_16; // For N = 16

reg [25:0] sign_in_26; // For N = 26

wire [31:0] sign_out_16;

wire [31:0] sign_out_26;

// N = 16

Sign_Extension_N_bit #(16) uut_16 (.sign_in(sign_in_16),.sign_out(sign_out_16));

// N = 26

Sign_Extension_N_bit #(26) uut_26 (.sign_in(sign_in_26),.sign_out(sign_out_26));

initial begin

\$display("\n-----Test Sign Extension N bit-----");

\$monitor("Time=%0t | N=16: sign_in=%b | sign_out=%b | N=26: sign_in=%b |
sign_out=%b",

\$time, sign_in_16, sign_out_16, sign_in_26, sign_out_26);

// Test Case 1: Positive input

sign_in_16 = 16'b0000_1111_0000_1111;

sign_in_26 = 26'b0000_0000_1111_0000_1111_0000_11;

#10;

// Test Case 2: Negative input

sign_in_16 = 16'b1111_1111_0000_1111;

sign_in_26 = 26'b1111_1111_1111_0000_1111_0000_11;

<pre> #10; // Test Case 3: Smallest negative value sign_in_16 = 16'b1000_0000_0000_0000; sign_in_26 = 26'b1000_0000_0000_0000_0000_0000_00; #10; // Test Case 4: Largest positive value sign_in_16 = 16'b0111_1111_1111_1111; sign_in_26 = 26'b0111_1111_1111_1111_1111_1111_11; #10; \$finish; end endmodule </pre>
Result
<pre> -----Test Sign Extension N bit----- Time=0 N=16: sign_in=0000111100001111 sign_out=0000000000000000111100001111 N=26: sign_in=00000000111100001111000011 sign_out=000000000000111100001111000011 Time=10 N=16: sign_in=1111111100001111 sign_out=1111111111111111111100001111 N=26: sign_in=11111111111100001111000011 sign_out=1111111111111111111100001111000011 Time=20 N=16: sign_in=1000000000000000 sign_out=111111111111110000000000000000 N=26: sign_in=10000000000000000000000000 sign_out=111111100000000000000000000000 Time=30 N=16: sign_in=0111111111111111 sign_out=000000000000000011111111111111 N=26: sign_in=01111111111111111111111111 sign_out=000000011111111111111111111111 jdoodle.v:47: \$finish called at 40 (1s) </pre>

2.8 ALU 16 Bits

Verilog code
<pre> // ALU 16bit module ALU_16bit(ALU_Sel, A, B, ALU_Out, zero); input [3:0] ALU_Sel; input [15:0] A; input [15:0] B; output reg [15:0] ALU_Out; </pre>

```

output reg zero;

parameter  ALU_OP_ADD      = 4'b0000, // Addition
           ALU_OP_SUB      = 4'b0001, // Subtraction
           ALU_OP_MUL      = 4'b0010, // Multiplication
           ALU_OP_DIV      = 4'b0011, // Division
           ALU_OP_AND      = 4'b0100, // Logical and
           ALU_OP_OR       = 4'b0101, // Logical or
           ALU_OP_XOR      = 4'b0110, // Logical xor
           ALU_OP_NOR      = 4'b0111, // Logical nor
           ALU_OP_NAND     = 4'b1000, // Logical nand
           ALU_OP_XNOR     = 4'b1001, // Logical xnor
           ALU_OP_SHL      = 4'b1010, // Logical shift left
           ALU_OP_SHR      = 4'b1011, // Logical shift right
           ALU_OP_ROL      = 4'b1100, // Rotate left
           ALU_OP_ROR      = 4'b1101, // Rotate right
           ALU_OP_BEQ      = 4'b1110, // Equal comparison
           ALU_OP_BNE      = 4'b1111; // Not Equal comparison

always @(*)
begin
    case(ALU_Sel)
        ALU_OP_ADD      : begin
                            zero=1'bx;
                            ALU_Out = A + B;
                        end
        ALU_OP_SUB      : ALU_Out = A - B;
        ALU_OP_MUL      : ALU_Out = A * B;
        ALU_OP_DIV      : ALU_Out = A / B;
        ALU_OP_AND      : ALU_Out = A & B;
        ALU_OP_OR       : ALU_Out = A | B;
        ALU_OP_XOR      : ALU_Out = A ^ B;
        ALU_OP_NOR      : ALU_Out = ~(A | B);
    endcase
end

```

```

        ALU_OP_NAND    : ALU_Out = ~(A & B);
        ALU_OP_XNOR    : ALU_Out = ~(A ^ B);
        ALU_OP_SHL     : ALU_Out = A<<1;
        ALU_OP_SHR     : ALU_Out = A>>1;
        ALU_OP_ROL     : ALU_Out = {A[6:0],A[7]};
        ALU_OP_ROR     : ALU_Out = {A[0],A[7:1]};
        ALU_OP_BEQ     : begin
                        zero = (A==B)?1'b1:1'b0;
                        ALU_Out = (A==B)?16'd1:16'd0;
                        end
        ALU_OP_BNE     : begin
                        zero = (A!=B)?1'b1:1'b0;
                        // zero here is different from the above zero
                        // zero here is equal to 1, when A is different from
B
                        // zero here is equal to 0, when A is the same as B
                        ALU_Out = (A!=B)?16'd1:16'd0;
                        end
        endcase
    end
endmodule

```

Testbench

```

// Testbench
module tb_ALU_16bit;

    reg [3:0] ALU_Sel;
    reg [15:0] A,B;
    wire [15:0] ALU_Out;
    wire zero;

```

```
ALU_16bit uut (.ALU_Sel(ALU_Sel),.A(A),.B(B),.ALU_Out(ALU_Out),.zero(zero));
```

```
initial begin
```

```
    $display("\n-----Test ALU 16 bit-----");
```

```
    $monitor("Time: %0t | ALU_Sel: %b | A: %h | B: %h | ALU_Out: %h | Zero: %b",  
            $time, ALU_Sel, A, B, ALU_Out, zero);
```

```
    A = 16'h0005;
```

```
    B = 16'h0003;
```

```
    ALU_Sel = 4'b0000; #10; // Addition
```

```
    ALU_Sel = 4'b0001; #10; // Subtraction
```

```
    ALU_Sel = 4'b0010; #10; // Multiplication
```

```
    ALU_Sel = 4'b0011; #10; // Division
```

```
    ALU_Sel = 4'b0100; #10; // Logical AND
```

```
    ALU_Sel = 4'b0101; #10; // Logical OR
```

```
    ALU_Sel = 4'b0110; #10; // Logical XOR
```

```
    ALU_Sel = 4'b0111; #10; // Logical NOR
```

```
    ALU_Sel = 4'b1000; #10; // Logical NAND
```

```
    ALU_Sel = 4'b1001; #10; // Logical XNOR
```

```
    ALU_Sel = 4'b1010; #10; // Logical Shift Left
```

```
    ALU_Sel = 4'b1011; #10; // Logical Shift Right
```

```
    ALU_Sel = 4'b1100; #10; // Rotate Left
```

```
    ALU_Sel = 4'b1101; #10; // Rotate Right
```

```
    ALU_Sel = 4'b1110; #10; // Equal Comparison
```

```
    ALU_Sel = 4'b1111; #10; // Not Equal Comparison
```

```
    $finish;
```

```
end
```

endmodule

Result

-----Test ALU 16 bit-----

```
Time: 0 | ALU_Sel: 0000 | A: 0005 | B: 0003 | ALU_Out: 0008 | Zero: x
Time: 10 | ALU_Sel: 0001 | A: 0005 | B: 0003 | ALU_Out: 0002 | Zero: x
Time: 20 | ALU_Sel: 0010 | A: 0005 | B: 0003 | ALU_Out: 000f | Zero: x
Time: 30 | ALU_Sel: 0011 | A: 0005 | B: 0003 | ALU_Out: 0001 | Zero: x
Time: 40 | ALU_Sel: 0100 | A: 0005 | B: 0003 | ALU_Out: 0001 | Zero: x
Time: 50 | ALU_Sel: 0101 | A: 0005 | B: 0003 | ALU_Out: 0007 | Zero: x
Time: 60 | ALU_Sel: 0110 | A: 0005 | B: 0003 | ALU_Out: 0006 | Zero: x
Time: 70 | ALU_Sel: 0111 | A: 0005 | B: 0003 | ALU_Out: fff8 | Zero: x
Time: 80 | ALU_Sel: 1000 | A: 0005 | B: 0003 | ALU_Out: fffe | Zero: x
Time: 90 | ALU_Sel: 1001 | A: 0005 | B: 0003 | ALU_Out: fff9 | Zero: x
Time: 100 | ALU_Sel: 1010 | A: 0005 | B: 0003 | ALU_Out: 000a | Zero: x
Time: 110 | ALU_Sel: 1011 | A: 0005 | B: 0003 | ALU_Out: 0002 | Zero: x
Time: 120 | ALU_Sel: 1100 | A: 0005 | B: 0003 | ALU_Out: 000a | Zero: x
Time: 130 | ALU_Sel: 1101 | A: 0005 | B: 0003 | ALU_Out: 0082 | Zero: x
Time: 140 | ALU_Sel: 1110 | A: 0005 | B: 0003 | ALU_Out: 0000 | Zero: 0
Time: 150 | ALU_Sel: 1111 | A: 0005 | B: 0003 | ALU_Out: 0001 | Zero: 1
jdoodle.v:40: $finish called at 160 (1s)
```

2.9 Completed Processor

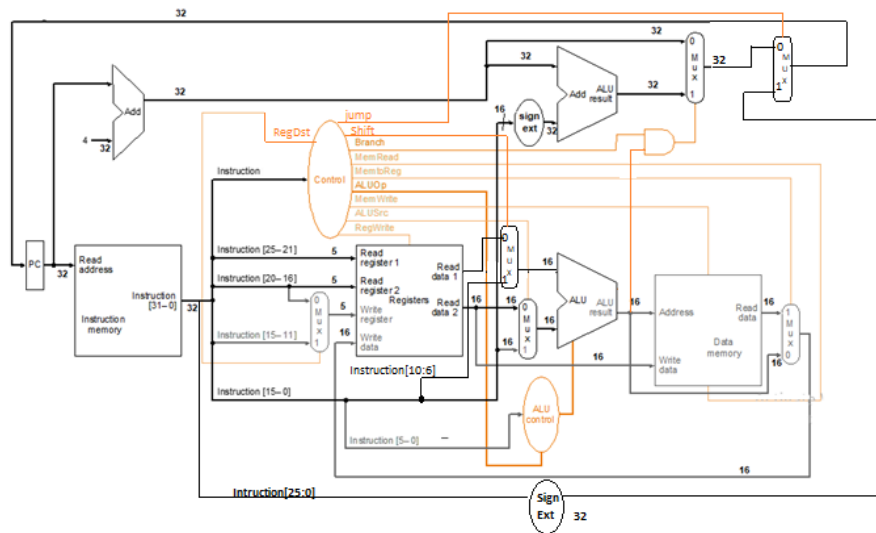


Figure 2.1 Single Cycle Microprocessor Schematic

Top module

```
module test(SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7);
    input [17:0]SW;
    output [17:0]LEDR;
    output [7:0]LEDG;
    output [0:6] HEX7, HEX6, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
    wire [31:0] W_PC_out,W_LED_SEG, W_m2;
    wire [15:0] W_RD1, W_RD2, W_m1, W_ALUout;

    assign LEDR=SW;
    hex_ssd (W_RD1 [3:0], HEX0);
    hex_ssd (W_RD1[7:4], HEX1);
    hex_ssd ( W_RD2[3:0],HEX2);
    hex_ssd ( W_RD2[7:4],HEX3);
    hex_ssd (W_PC_out[3:0],HEX4);
    hex_ssd (W_PC_out[7:4],HEX5);
    hex_ssd (W_ALUout[3:0],HEX6);
    hex_ssd (W_ALUout[7:4],HEX7);

    Single_Cycle_Processor_16bit(.reset(SW[0]),.clk(SW[1]),.W_PC_out(W_PC_out),.in
struction(W_LED_SEG),.W_RD1(W_RD1),.W_RD2(W_RD2),.W_m1(W_m1),.W_m2(W_
m2),.W_ALUout(W_ALUout));
endmodule
module hex_ssd (BIN, SSD);
    input [3:0] BIN;
    output reg [0:6] SSD;

    always begin
        case(BIN)
```

```

        0:SSD=7'b00000001;
        1:SSD=7'b10011111;
        2:SSD=7'b0010010;
        3:SSD=7'b0000110;
        4:SSD=7'b1001100;
        5:SSD=7'b0100100;
        6:SSD=7'b0100000;
        7:SSD=7'b0001111;
        8:SSD=7'b0000000;
        9:SSD=7'b0001100;
        10:SSD=7'b0001000;
        11:SSD=7'b1100000;
        12:SSD=7'b0110001;
        13:SSD=7'b1000010;
        14:SSD=7'b0110000;
        15:SSD=7'b0111000;

    endcase

end

endmodule

```

Verilog code

```

//Single Cycle Processor 16bit
module Single_Cycle_Processor_16bit(reset, clk,W_PC_out, instruction, W_RD1,
W_RD2,W_m1,W_m2,W_ALUout);
    input reset, clk;
    output [31:0] W_PC_out, instruction, W_m2;
    output [15:0] W_RD1, W_RD2, W_m1, W_ALUout;
    wire [31:0] W_PC_in,W_PC_plus_1,W_Branch_add,W_m4,W_jump_PC;
    wire
PCsrc,RegWrite,zero,ALUsrc,MemRead,MemWrite,MemtoReg,RegDst,Branch,jump,shift;
    wire [15:0] W_MemtoReg,W_RD1,W_RD2,W_ALUout,W_m1,W_RDm,W_m5;
    wire [3:0] ALUop;

```

```

        wire [4:0] W_m3;

        Program_Counter                                C1(.clk(clk),.reset(reset),.PC_in(
W_PC_plus_1),.PC_out(W_PC_out));
        Adder32Bit                                     C2(.input1(W_PC_out),.input2(32'd1),.out(W_PC_plus_1));
        Mux_32_bit
C3(.in0(W_PC_plus_1),.in1(W_m2),.mux_out(W_m4),.select(PCsrc));
        Mux_32_bit
C4(.in0(W_m4),.in1(W_jump_PC),.mux_out(W_PC_in),.select(jump));
        Adder32Bit      C5(.input1(W_PC_plus_1),.input2(W_Branch_add),.out(W_m2));
        Instruction_Memory
C6(.read_address(W_PC_out),.instruction(instruction),.reset(reset));
        Register_File_16bit
C7(.clk(clk),.read_addr_1(instruction[25:21]),.read_addr_2(instruction[20:16]),.write_addr(W
_m3),.write_data(W_MemtoReg),.RegWrite(RegWrite),.read_data_1(W_RD1),.read_data_2(
W_RD2));
        Sign_Extension_16  C8(.sign_in(instruction[15:0]),.sign_out(W_Branch_add));
        Mux_16_bit
C9(.in0(W_RD2),.in1(instruction[15:0]),.mux_out(W_m1),.select(ALUsrc));
        Mux_16_bit
C10(.in0(W_RD1),.in1(instruction[15:0]),.mux_out(W_m5),.select(shift));
        ALU_16bit
        C11(.ALU_Sel(ALUop),.A(W_m5),.B(W_m1),.ALU_Out(W_ALUout),.zero(zero));
        Data_Memory_16bit
C12(.clk(clk),.addr(W_ALUout),.write_data(W_RD2),.read_data(W_RDm),.MemRead(Mem
Read),.MemWrite(MemWrite));
        Mux_16_bit
C13(.in0(W_ALUout),.in1(W_RDm),.mux_out(W_MemtoReg),.select(MemtoReg));
        Sign_Extension_26  C14(.sign_in(instruction[25:0]),.sign_out(W_jump_PC));
        Control
C15(.clk(clk),.Op_intstruct(instruction[31:26]),.ints_function(instruction[5:0]),

```



```

.RegDst(RegDst),.Branch(Branch),.MemRead(MemRead),.MemtoReg(MemtoReg),.ALUOp(
ALUOp),.MemWrite(MemWrite),.ALUSrc(ALUSrc),.RegWrite(RegWrite),.Zero(zero),.Jump
(jump),.Shift(shift));
    Mux_5_bit
C16(.in0(instruction[20:16]),.in1(instruction[15:11]),.mux_out(W_m3),.select(RegDst));
    and                                C17(PCsrc,Branch,zero);
endmodule

// Control
module Control(clk, Op_intstruct, ints_function, RegDst, Branch, MemRead, MemtoReg,
ALUOp, MemWrite, ALUSrc, RegWrite, Zero, Jump,Shift);
    input clk,Zero;
    input [5:0] ints_function;
    input [5:0] Op_intstruct;
    output                                           reg
RegDst,Branch,MemRead,MemtoReg,Jump,MemWrite,ALUSrc,RegWrite,Shift;
    output reg [3:0] ALUOp;
    always @(*)
    begin
        case (Op_intstruct)
            6'b000000: begin // R-Type Instruction
                RegDst = 1;
                Jump = 0;
                Branch = 0;
                MemRead = 0;
                MemtoReg = 0;
                MemWrite = 0;
                ALUSrc = 0;
                RegWrite = 1;
                Shift =0;
                case (ints_function)

```

```

6'b100000: ALUOp = 4'b0000; // Addition
6'b100010: ALUOp = 4'b0001; // Subtraction
6'b011000: ALUOp = 4'b0010; // Multiplication
6'b011010: ALUOp = 4'b0011; // Division
6'b100100: ALUOp = 4'b0100; // Logical AND
6'b100101: ALUOp = 4'b0101; // Logical OR
6'b100110: ALUOp = 4'b0110; // Logical XOR
6'b100111: ALUOp = 4'b0111; // Logical NOR
6'b101000: ALUOp = 4'b1000; // Logical NAND
6'b101010: ALUOp = 4'b1001; // Logical XNOR
6'b000000: begin // Logical Shift Left
    ALUOp = 4'b1010;
    Shift = 1;
end
6'b000010: begin // Logical Shift Right
    ALUOp = 4'b1011;
    Shift = 1;
end
6'b111000: begin // Rotate Left (ROL)
    ALUOp = 4'b1100;
    Shift = 1;
end
6'b110000: begin // Rotate Right (ROR)
    ALUOp = 4'b1101;
    Shift = 1;
end
default: ALUOp = 4'b0000;
endcase
end
// I-Type Instruction
6'b000100: begin // BEQ

```

```

    RegDst = 0;
    Jump = 0;
    Branch = (Zero == 1) ? 1 : 0;
    MemRead = 0;
    MemtoReg = 0;
    ALUOp = 4'b1110;
    MemWrite = 0;
    ALUSrc = 0;
    RegWrite = 0;
    Shift = 0;

```

```
end
```

```
6'b100011: begin // LW
```

```

    RegDst = 0;
    Jump = 0;
    Branch = 0;
    MemRead = 1;
    MemtoReg = 1;
    ALUOp = 4'b0000;
    MemWrite = 0;
    ALUSrc = 1;
    RegWrite = 1;
    Shift = 0;

```

```
end
```

```
6'b101011: begin // SW
```

```

    RegDst = 0;
    Jump = 0;
    Branch = 0;
    MemRead = 0;
    MemtoReg = 0;
    ALUOp = 4'b0000;
    MemWrite = 1;

```

```

        ALUSrc = 1;
        RegWrite = 0;
        Shift =0;
    end
    6'b001000: begin // ADDI
        RegDst = 0;
        Jump = 0;
        Branch = 0;
        MemRead = 0;
        MemtoReg = 0;
        ALUOp = 4'b0000;
        MemWrite = 0;
        ALUSrc = 1;
        RegWrite = 1;
                Shift =0;
    end
    6'b000101: begin // BNE
        RegDst = 0;
        Jump = 0;
        Branch = (Zero == 0) ? 1 : 0;
        MemRead = 0;
        MemtoReg = 0;
        ALUOp = 4'b1111;
        MemWrite = 0;
        ALUSrc = 0;
        RegWrite = 0;
                Shift =0;
    end

        // J-Type Instruction
    6'b000010: begin // JUMP
        RegDst = 0;

```

```

    Jump = 1;
    Branch = 0;
    MemRead = 0;
    MemtoReg = 0;
    ALUOp = 4'b0000;
    MemWrite = 0;
    ALUSrc = 1;
    RegWrite = 0;

                                Shift =0;
end
6'b000011: begin // JUMP and LINK
                                RegDst= 1;
                                Jump = 1;
                                Branch = 0;
                                MemRead = 0;
                                MemtoReg = 1;
                                ALUOp = 4'b0000;
                                MemWrite= 0;
                                ALUSrc = 0;
                                RegWrite = 1;
                                Shift =0;
                                end
                                default: begin // Default case
    RegDst = 0;
    Branch = 0;
    Jump = 0;
    MemRead = 0;
    MemtoReg = 0;
    ALUOp = 4'b0000;
    MemWrite = 0;
    ALUSrc = 0;

```

```

        RegWrite = 0;

        Shift =0;

    end

endcase

end

endmodule

// Register File 16bit
module Register_File_16bit (clk,read_addr_1, read_addr_2, write_addr, write_data,
RegWrite,read_data_1, read_data_2);
    input clk,RegWrite;
    input [4:0] read_addr_1, read_addr_2, write_addr;
    input [15:0] write_data;
    output [15:0] read_data_1, read_data_2;
    reg [15:0] Regfile [31:0];
    integer i;

    initial begin
        for (i = 0; i < 32; i = i + 1) begin
            Regfile[i] = 16'b0;
        end
        Regfile[19]=1; // $s3 = 1
        Regfile[17]=3; // $s1 = 3
        Regfile[20]=2; // $s4 = 2
        Regfile[21]=5; // $s5 = 5
    end

    assign read_data_1 = Regfile[read_addr_1];
    assign read_data_2 = Regfile[read_addr_2];

```

```

always @(posedge clk) begin
    if (RegWrite) begin
        Regfile[write_addr] <= write_data;
        //$display("write_addr=%h
write_data=%h",write_addr,write_data);
    end
end
endmodule

// ALU 16bit
module ALU_16bit(ALU_Sel, A, B, ALU_Out, zero);
    input [3:0] ALU_Sel;
    input [15:0] A;
    input [15:0] B;
    output reg [15:0] ALU_Out;
    output reg zero;
    parameter    ALU_OP_ADD      = 4'b0000, // Addition
                  ALU_OP_SUB      = 4'b0001, // Subtraction
                  ALU_OP_MUL      = 4'b0010, // Multiplication
                  ALU_OP_DIV      = 4'b0011, // Division
                  ALU_OP_AND      = 4'b0100, // Logical and
                  ALU_OP_OR       = 4'b0101, // Logical or
                  ALU_OP_XOR      = 4'b0110, // Logical xor
                  ALU_OP_NOR      = 4'b0111, // Logical nor
                  ALU_OP_NAND     = 4'b1000, // Logical nand
                  ALU_OP_XNOR     = 4'b1001, // Logical xnor
                  ALU_OP_SHL      = 4'b1010, // Logical shift left
                  ALU_OP_SHR      = 4'b1011, // Logical shift right
                  ALU_OP_ROL      = 4'b1100, // Rotate left
                  ALU_OP_ROR      = 4'b1101, // Rotate right

```

```

        ALU_OP_BEQ      = 4'b1110, // Equal comparison
        ALU_OP_BNE     = 4'b1111; // Not Equal comparison

always @(*)
    begin
        case(ALU_Sel)
            ALU_OP_ADD      : begin
                                zero=1'bx;
                                ALU_Out = A + B;
                            end
            ALU_OP_SUB      : ALU_Out = A - B;
            ALU_OP_MUL      : ALU_Out = A * B;
            ALU_OP_DIV      : ALU_Out = A / B;
            ALU_OP_AND      : ALU_Out = A & B;
            ALU_OP_OR       : ALU_Out = A | B;
            ALU_OP_XOR      : ALU_Out = A ^ B;
            ALU_OP_NOR      : ALU_Out = ~(A | B);
            ALU_OP_NAND     : ALU_Out = ~(A & B);
            ALU_OP_XNOR     : ALU_Out = ~(A ^ B);
            ALU_OP_SHL      : ALU_Out = A<<1;
            ALU_OP_SHR      : ALU_Out = A>>1;
            ALU_OP_ROL      : ALU_Out = {A[6:0],A[7]};
            ALU_OP_ROR      : ALU_Out = {A[0],A[7:1]};
            ALU_OP_BEQ      : begin
                                zero = (A==B)?1'b1:1'b0;
                                ALU_Out =
(A==B)?16'd1:16'd0;
                            end
            ALU_OP_BNE      : begin
                                zero = (A!=B)?1'b1:1'b0;
                                // zero here is different from the
                                above zero
                            end
        end
    end

```



```

// zero here is equal to 1, when A
is different from B

// zero here is equal to 0, when A
is the same as B

ALU_Out =
(A!=B)?16'd1:16'd0;

end

endcase

end

endmodule

```

// Sign Extension 16 bit

```

module Sign_Extension_16 (sign_in, sign_out);
    parameter N = 16;
    input [N-1:0] sign_in;
    output [31:0] sign_out;

    assign sign_out = {{(32-N){sign_in[N-1]}}, sign_in};
endmodule

```

// Sign Extension 26 bit

```

module Sign_Extension_26 (sign_in, sign_out);
    parameter N = 26;
    input [N-1:0] sign_in;
    output [31:0] sign_out;

    assign sign_out = {{(32-N){sign_in[N-1]}}, sign_in};
endmodule

```

```

// Adder 32 bit
module Adder32Bit(input1, input2, out);
    input [31:0] input1, input2;
    output [31:0] out;
    reg [31:0]out;
    always@( input1 or input2)
        begin
            out <= input1 + input2;
        end
endmodule

// Program Counter
module Program_Counter(clk, reset, PC_in, PC_out);
    input clk, reset;
    input [31:0] PC_in;
    output reg [31:0] PC_out;

    always @(posedge clk) begin
        if(reset)
            PC_out <= 32'b0;
        else
            PC_out <= PC_in;
        end
    endmodule

// Mux 32_bit
module Mux_32_bit (in0, in1, mux_out, select);
    parameter N=32;

```

```

        input [N-1:0] in0, in1;
        output [N-1:0] mux_out;
        input select;
        assign mux_out = select ? in1 : in0;
endmodule

// Mux 16 bit
module Mux_16_bit (in0, in1, mux_out, select);
    parameter N=16;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select ? in1 : in0;
endmodule

// Mux 5 bit
module Mux_5_bit (in0, in1, mux_out, select);
    parameter N=5;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select ? in1 : in0;
endmodule

//Data Memory 16 bit
module Data_Memory_16bit (clk,addr,write_data,read_data,MemRead,MemWrite);
    input clk;
    input [15:0] addr;

```

```

input [15:0] write_data;
output reg [15:0] read_data;
input MemRead;
input MemWrite;
integer i;
reg [15:0] DMemory [0:255];

initial begin
    for (i = 0; i < 256; i = i + 1) begin
        DMemory[i] = 16'h0000;
    end
end

always @(posedge clk) begin
    if (MemWrite) begin
        DMemory[addr] <= write_data;
        //$display("Memory Write: Address=%h Data=%h", addr, write_data);
    end
end

always @(*) begin
    if (MemRead)
        read_data = DMemory[addr];
    else
        read_data = 16'h0000;
    end
endmodule

// Instruction Memory
module Instruction_Memory (read_address, instruction, reset);

```

```

input reset;
input [31:0] read_address;
output [31:0] instruction;
reg [31:0] Imemory [256:0];
integer i;
assign instruction = Imemory[read_address];
always @(posedge reset)
begin
for (i=0; i<32; i=i+1)
    begin
        Imemory[i] = 32'b0;
    end
/*Test R-type*/
// add $s6, $s5, $s4      R22 = R21 + R20 = 0x7 (0x5 + 0x2)
Imemory[0] = 32'b000000_10101_10100_10110_00000_100000;
// sub $s6, $s5, $s4      R22 = R21 - R20 = 0x3 (0x5 - 0x2)
Imemory[1] = 32'b000000_10101_10100_10110_00000_100010;
// mult $s5, $s4          R21 * R20 = 0xA (0x5 * 0x2)
Imemory[2] = 32'b000000_10101_10100_00000_00000_011000;
// div $s5, $s4           R21 / R20 = 0x2 (0x5 / 0x2)
Imemory[3] = 32'b000000_10101_10100_00000_00000_011010;
// and $s6, $s5, $s4      R22 = AND(R21, R20) = 0x0 (0x5 AND 0x2)
Imemory[4] = 32'b000000_10101_10100_10110_00000_100100;
// or $s6, $s5, $s4       R22 = OR(R21, R20) = 0x7 (0x5 OR 0x2)
Imemory[5] = 32'b000000_10101_10100_10110_00000_100101;
// xor $s6, $s5, $s4      R22 = XOR(R21, R20) = 0x7 (0x5 XOR 0x2)
Imemory[6] = 32'b000000_10101_10100_10110_00000_100110;
// nor $s6, $s5, $s4      R22 = NOR(R21, R20) = 0xFFFFFFF8 (NOR of 0x5
and 0x2)

Imemory[7] = 32'b000000_10101_10100_10110_00000_100111;
// nand $s6, $s5, $s4     R22 = NAND(R21, R20) = 0xFFFFFFF8 (NAND of

```

0x5 and 0x2)

```
Imemory[8] = 32'b000000_10101_10100_10110_00000_101000;
```

```
// xnor $s6, $s5, $s4      R22 = XNOR(R21, R20) = 0xFFFFFFF0 (XNOR of
```

0x5 and 0x2)

```
Imemory[9] = 32'b000000_10101_10100_10110_00000_101010;
```

```
// sll $s6, $s5, $s4      R22 = R21 << R20 = 0x14 (0x5 << 0x2)
```

```
Imemory[10] = 32'b000000_10101_10100_10110_00000_000000;
```

```
// srl $s6, $s5, $s4      R22 = R21 >> R20 = 0x1 (0x5 >> 0x2)
```

```
Imemory[11] = 32'b000000_10101_10100_10110_00000_000010;
```

```
// rol $s6, $s5           R22 = R21 rotated 1 bit left = 0xA (rotate 0x5 left by 1)
```

```
Imemory[12] = 32'b000000_10101_00000_10110_00000_111000;
```

```
// ror $s6, $s5           R22 = R21 rotated 1 bit right = 0x2 (rotate 0x5 right by
```

1)

```
Imemory[13] = 32'b000000_10101_00000_10110_00000_110000;
```

```
/*Test I-type*/
```

```
// addi $s1, $s1, 0x05     R17 = 0x4E => R17 = R17 + 0x5 = 0x53
```

```
Imemory[14] = 32'b001000_10001_10001_00000_00000_000101;
```

```
// addi $s1, $s1, 0x05     R17 = 0x53 => R17 = R17 + 0x5 = 0x58
```

```
Imemory[15] = 32'b001000_10001_10001_00000_00000_000101;
```

```
// addi $s3, $s1, 0x10     R17 = 0x58 => R19 = R17 + 0x10 = 0x68
```

```
Imemory[16] = 32'b001000_10001_10011_00000_00000_010000;
```

```
// sw $s3, 0x04($s1)      Memory[$s1 + 0x04] = $s3 => Memory[0x58 + 0x04] = 0x68
```

```
Imemory[17] = 32'b101011_10001_10011_00000_00000_000100;
```

```
// lw $s7, 0x04($s1)      $s7 = Memory[$s1 + 0x04] = 0x68
```

```
Imemory[18] = 32'b100011_10001_10111_00000_00000_000100;
```

```
// beq $s7, $s3, 0x08     R23 (0x68) == R19 (0x68) move to Imemory[22 + 8 + 1]
```

```
Imemory[19] = 32'b000100_10111_10011_00000_00000_001000;
```

```
// addi $s1, $zero, 0x11   R17 = 0x11
```

```
Imemory[20] = 32'b001000_00000_10001_00000_00000_010001;
```

```
// addi $s1, $zero, 0x22   R17 = 0x22
```

```

Imemory[21] = 32'b001000_00000_10001_00000_00000_100010;
// addi $s1, $zero, 0x33    R17 = 0x33
Imemory[22] = 32'b001000_00000_10001_00000_00000_110011;
// bne $s1, $s7, 0x04      (R17 (0x33) != R23 (0x68)) move to Imemory[26 + 4 + 1]
Imemory[23] = 32'b000101_10001_10111_00000_00000_000100;
// addi $s2, $zero, 0x66    R18 = 0x66
Imemory[24] = 32'b001000_00000_10010_00000_00001_100110;
// addi $s2, $zero, 0x77    R18 = 0x77
Imemory[25] = 32'b001000_00000_10010_00000_00001_110111;

/* Test J-type */
    // j 0x74 (JUMP to Imemory[116])
    Imemory[26] = 32'b000010_00000_00000_00000_00001_110100;
    // jal 0x74 (Jump and Link to Imemory[116])
    Imemory[27] = 32'b000011_00000_00000_00000_00001_110100;
    // j 0x78 (JUMP to Imemory[120])
    Imemory[28] = 32'b000010_00000_00000_00000_00001_111000;
    // jal 0x78 (Jump and Link to Imemory[120])
    Imemory[29] = 32'b000011_00000_00000_00000_00001_111000;
    // j 0x64 (JUMP to Imemory[100])
    Imemory[30] = 32'b000010_00000_00000_00000_00001_100100;
    // jal 0x68 (Jump and Link to Imemory[104])
    Imemory[31] = 32'b000011_00000_00000_00000_00001_101000;
    // j 0x6C (JUMP to Imemory[108])
    Imemory[32] = 32'b000010_00000_00000_00000_00001_101100;
    // jal 0x70 (Jump and Link to Imemory[112])
    Imemory[33] = 32'b000011_00000_00000_00000_00001_110000;
    // j 0x74 (JUMP to Imemory[116])
    Imemory[34] = 32'b000010_00000_00000_00000_00001_110100;
    // j 0x7C (JUMP to Imemory[124])
    Imemory[35] = 32'b000010_00000_00000_00000_00001_111100;

```

```
end  
endmodule
```

Testbench

```
// Testbench  
module tb_Single_Cycle_Processor;  
    reg reset, clk;  
    wire [31:0] W_PC_out, instruction, W_m2;  
    wire [15:0] W_RD1, W_RD2, W_m1, W_ALUout;  
    reg [127:0] instr_name;  
  
    Single_Cycle_Processor_16bit dut(  
        .reset(reset),  
        .clk(clk),  
        .W_PC_out(W_PC_out),  
        .instruction(instruction),  
        .W_RD1(W_RD1),  
        .W_RD2(W_RD2),  
        .W_m1(W_m1),  
        .W_m2(W_m2),  
        .W_ALUout(W_ALUout)  
    );  
  
    always #5 clk = ~clk;  
  
    always @(instruction) begin  
        case (instruction[31:26])  
            6'b000000: begin
```



```

        case (instruction[5:0]) // funct field
            6'b100000: instr_name = "ADD    ";
            6'b100010: instr_name = "SUB    ";
            6'b011000: instr_name = "MULT   ";
            6'b011010: instr_name = "DIV    ";
            6'b100100: instr_name = "AND    ";
            6'b100101: instr_name = "OR     ";
            6'b100110: instr_name = "XOR    ";
            6'b100111: instr_name = "NOR    ";
            6'b101000: instr_name = "NAND   ";
            6'b101010: instr_name = "XNOR   ";
            6'b000000: instr_name = "SLL    ";
            6'b000010: instr_name = "SRL    ";
            6'b111000: instr_name = "ROL    ";
            6'b110000: instr_name = "ROR    ";
            default: instr_name = "UNKNOWN_R ";
        endcase
    end

    6'b000100: instr_name = "BEQ     ";
    6'b100011: instr_name = "LW      ";
    6'b101011: instr_name = "SW      ";
    6'b001000: instr_name = "ADDI    ";
    6'b000101: instr_name = "BNE     ";
    6'b000010: instr_name = "J       ";
    6'b000011: instr_name = "JAL     ";
    default: instr_name = "UNKNOWN  ";
endcase
end

always @(posedge clk) begin
    $display($time,

```

```

        " reset=%b | clk=%b | PC=%4d | Inst=%-10s | Op=%6b | rs=%2d | rt=%2d | rd=%2d |
zero=%b | Imm=%4h | ALU=%4h | RD1=%4h | RD2=%4h",
        reset, clk, W_PC_out, instr_name, instruction[31:26],
        instruction[25:21], instruction[20:16], instruction[15:11],
        dut.C11.zero, instruction[15:0], W_ALUout, W_RD1, W_RD2);
end

initial begin
    clk = 0;
    reset = 1;
    instr_name = "";

    $display("\n\t\t\t\t-----TEST SINGLE-CYCLE PROCESSOR-----\n");
    $display("\n\t\t\t\t-----R-TYPE INSTRUCTIONS TEST-----\n");

    #10 reset = 0;
    #10 reset = 1;
    #140 $display("\n\t\t\t\t\t-----I-TYPE INSTRUCTIONS TEST-----\n");

    #120 $display("\n\t\t\t\t\t-----J-TYPE INSTRUCTIONS TEST-----\n");

    #100 $finish;
end
endmodule

```

```

-----TEST SINGLE-CYCLE PROCESSOR-----

-----R-TYPE INSTRUCTIONS TEST-----

 5 reset=0 | clk=1 | PC= 0 | Inst=      | Op=xxxxxx | rs= x | rt= x | rd= x | zero=x | Imm=xxxx | ALU=xxxx | RD1=xxxx | RD2=xxxx
15 reset=1 | clk=1 | PC= 1 | Inst=SUB | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b022 | ALU=0003 | RD1=0005 | RD2=0002
25 reset=0 | clk=1 | PC= 0 | Inst=ADD | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b020 | ALU=0007 | RD1=0005 | RD2=0002
35 reset=0 | clk=1 | PC= 1 | Inst=SUB | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b022 | ALU=0003 | RD1=0005 | RD2=0002
45 reset=0 | clk=1 | PC= 2 | Inst=MULT | Op=000000 | rs=21 | rt=20 | rd= 0 | zero=x | Imm=0018 | ALU=000a | RD1=0005 | RD2=0002
55 reset=0 | clk=1 | PC= 3 | Inst=DIV | Op=000000 | rs=21 | rt=20 | rd= 0 | zero=x | Imm=001a | ALU=0002 | RD1=0005 | RD2=0002
65 reset=0 | clk=1 | PC= 4 | Inst=AND | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b024 | ALU=0000 | RD1=0005 | RD2=0002
75 reset=0 | clk=1 | PC= 5 | Inst=OR | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b025 | ALU=0007 | RD1=0005 | RD2=0002
85 reset=0 | clk=1 | PC= 6 | Inst=XOR | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b026 | ALU=0007 | RD1=0005 | RD2=0002
95 reset=0 | clk=1 | PC= 7 | Inst=NOR | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b027 | ALU=ffff | RD1=0005 | RD2=0002
105 reset=0 | clk=1 | PC= 8 | Inst=NAND | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b028 | ALU=ffff | RD1=0005 | RD2=0002
115 reset=0 | clk=1 | PC= 9 | Inst=XNOR | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b02a | ALU=ffff | RD1=0005 | RD2=0002
125 reset=0 | clk=1 | PC=10 | Inst=SLL | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b000 | ALU=6000 | RD1=0005 | RD2=0002
135 reset=0 | clk=1 | PC=11 | Inst=SRL | Op=000000 | rs=21 | rt=20 | rd=22 | zero=x | Imm=b002 | ALU=5001 | RD1=0005 | RD2=0002
145 reset=0 | clk=1 | PC=12 | Inst=ROL | Op=000000 | rs=21 | rt= 0 | rd=22 | zero=x | Imm=b038 | ALU=0070 | RD1=0005 | RD2=0002
155 reset=0 | clk=1 | PC=13 | Inst=ROL | Op=000000 | rs=21 | rt= 0 | rd=22 | zero=x | Imm=b030 | ALU=0018 | RD1=0005 | RD2=0002

-----I-TYPE INSTRUCTIONS TEST-----


165 reset=0 | clk=1 | PC= 14 | Inst=ADDI | Op=001000 | rs=17 | rt=17 | rd= 0 | zero=x | Imm=0005 | ALU=0008 | RD1=0003 | RD2=0003
175 reset=0 | clk=1 | PC= 15 | Inst=ADDI | Op=001000 | rs=17 | rt=17 | rd= 0 | zero=x | Imm=0005 | ALU=000d | RD1=0008 | RD2=0008
185 reset=0 | clk=1 | PC= 16 | Inst=ADDI | Op=001000 | rs=17 | rt=19 | rd= 0 | zero=x | Imm=0010 | ALU=001d | RD1=000d | RD2=0001
195 reset=0 | clk=1 | PC= 17 | Inst=SW | Op=101011 | rs=17 | rt=19 | rd= 0 | zero=x | Imm=0004 | ALU=0011 | RD1=000d | RD2=001d
205 reset=0 | clk=1 | PC= 18 | Inst=LW | Op=100011 | rs=17 | rt=23 | rd= 0 | zero=x | Imm=0004 | ALU=0011 | RD1=000d | RD2=0000
215 reset=0 | clk=1 | PC= 19 | Inst=BEQ | Op=000100 | rs=23 | rt=19 | rd= 0 | zero=1 | Imm=0008 | ALU=0001 | RD1=001d | RD2=001d
225 reset=0 | clk=1 | PC= 20 | Inst=ADDI | Op=001000 | rs= 0 | rt=17 | rd= 0 | zero=x | Imm=0011 | ALU=0013 | RD1=0002 | RD2=000d
235 reset=0 | clk=1 | PC= 21 | Inst=ADDI | Op=001000 | rs= 0 | rt=17 | rd= 0 | zero=x | Imm=0022 | ALU=0024 | RD1=0002 | RD2=0013
245 reset=0 | clk=1 | PC= 22 | Inst=ADDI | Op=001000 | rs= 0 | rt=17 | rd= 0 | zero=x | Imm=0033 | ALU=0035 | RD1=0002 | RD2=0024
255 reset=0 | clk=1 | PC= 23 | Inst=BNE | Op=000101 | rs=17 | rt=23 | rd= 0 | zero=1 | Imm=0004 | ALU=0001 | RD1=0035 | RD2=001d
265 reset=0 | clk=1 | PC= 24 | Inst=ADDI | Op=001000 | rs= 0 | rt=18 | rd= 0 | zero=x | Imm=0066 | ALU=0068 | RD1=0002 | RD2=0000
275 reset=0 | clk=1 | PC= 25 | Inst=ADDI | Op=001000 | rs= 0 | rt=18 | rd= 0 | zero=x | Imm=0077 | ALU=0079 | RD1=0002 | RD2=0068

-----J-TYPE INSTRUCTIONS TEST-----


285 reset=0 | clk=1 | PC= 26 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0074 | ALU=0076 | RD1=0002 | RD2=0002
295 reset=0 | clk=1 | PC= 27 | Inst=JAL | Op=000011 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0074 | ALU=0004 | RD1=0002 | RD2=0002
305 reset=0 | clk=1 | PC= 28 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0078 | ALU=0078 | RD1=0000 | RD2=0000
315 reset=0 | clk=1 | PC= 29 | Inst=JAL | Op=000011 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0078 | ALU=0000 | RD1=0000 | RD2=0000
325 reset=0 | clk=1 | PC= 30 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0064 | ALU=0064 | RD1=0000 | RD2=0000
335 reset=0 | clk=1 | PC= 31 | Inst=JAL | Op=000011 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0068 | ALU=0000 | RD1=0000 | RD2=0000
345 reset=0 | clk=1 | PC= 32 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=006c | ALU=006c | RD1=0000 | RD2=0000
355 reset=0 | clk=1 | PC= 33 | Inst=JAL | Op=000011 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0070 | ALU=0000 | RD1=0000 | RD2=0000
365 reset=0 | clk=1 | PC= 34 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=0074 | ALU=0074 | RD1=0000 | RD2=0000
375 reset=0 | clk=1 | PC= 35 | Inst=J | Op=000010 | rs= 0 | rt= 0 | rd= 0 | zero=x | Imm=007c | ALU=007c | RD1=0000 | RD2=0000

```


R-Type

 

I-Type

 

J-Type

 

5	reset=0	clk=1	PC= 0	Inst=	Op=xxxxxx	rs= x	rt= x	rd= x	zero=x	Imm=xxxx	ALU=xxxx	RD1=xxxx	RD2=xxxx
15	reset=1	clk=1	PC= 1	Inst=SUB	Op=000000	rs=21	rt=20	rd=22	zero=x	Imm=b022	ALU=0003	RD1=0005	RD2=0002
25	reset=0	clk=1	PC= 0	Inst=ADD	Op=000000	rs=21	rt=20	rd=22	zero=x	Imm=b020	ALU=0007	RD1=0005	RD2=0002
35	reset=0	clk=1	PC= 1	Inst=SUB	Op=000000	rs=21	rt=20	rd=22	zero=x	Imm=b022	ALU=0003	RD1=0005	RD2=0002
45	reset=0	clk=1	PC= 2	Inst=ADDI	Op=001000	rs=17	rt=17	rd= 0	zero=x	Imm=0005	ALU=0008	RD1=0003	RD2=0003
55	reset=0	clk=1	PC= 3	Inst=ADDI	Op=001000	rs=17	rt=17	rd= 0	zero=x	Imm=0005	ALU=000d	RD1=0008	RD2=0008
65	reset=0	clk=1	PC= 4	Inst=J	Op=000010	rs= 0	rt= 0	rd= 0	zero=x	Imm=0074	ALU=0074	RD1=0000	RD2=0000
75	reset=0	clk=1	PC= 5	Inst=JAL	Op=000011	rs= 0	rt= 0	rd= 0	zero=x	Imm=0074	ALU=0000	RD1=0000	RD2=0000

I use the results of this testbench to verify the outcomes on the FBGA because there is no debouncing in the SWing button. As a result, during operation, the register values may change, leading to incorrect results. Therefore, I modified the first 6 commands to test all three types (R, I, J).