

II. PROCEDURE

II.1 LAB EXPERIMENT 1 : WRITE VHDL CODE TO IMPLEMENT ALL LOGIC GATES IN FPGA KIT.

AND GATE




A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

NOT GATE

 

A	\bar{A}
0	1
1	0

NAND GATE



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

XOR GATE



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

XNOR GATE



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

Top module

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Simple module that connects the SW switches to the LEDR lights
ENTITY lab4_ex1 IS
PORT (SW      : IN  STD_LOGIC_VECTOR(17 DOWNTO 0);
      LEDR    : OUT STD_LOGIC_VECTOR(17 DOWNTO 0);
      LEDG    : OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END lab4_ex1;

ARCHITECTURE Structure OF lab4_ex1 IS
    COMPONENT all_gates
        PORT (A: in std_logic;
```



<pre>B: in std_logic; Y_AND: out std_logic; Y_OR: out std_logic; Y_NOT_A: out std_logic; Y_NAND: out std_logic; Y_NOR: out std_logic; Y_XOR: out std_logic; Y_XNOR: out std_logic); END COMPONENT; BEGIN LEDR <= SW; DUT: all_gates PORT MAP(SW(1),SW(0),LEDG(6),LEDG(5),LEDG(4),LEDG(3),LEDG(2),LEDG(1),LEDG(0)); END Structure;</pre>		
Structural	Dataflow	Behavior
<pre>library IEEE; use IEEE.STD_LOGIC_1164.ALL; entity all_gates is port(A: in std_logic; B: in std_logic; Y_AND: out std_logic; Y_OR: out std_logic; Y_NOT_A: out std_logic; Y_NAND: out std_logic; Y_NOR: out std_logic; Y_XOR: out std_logic; Y_XNOR: out std_logic); end all_gates; architecture structural of all_gates is -- Declare components for each gate component AND_GATE port (A, B: in std_logic; Y: out std_logic); end component; component OR_GATE port (A, B: in std_logic; Y: out std_logic); end component; component NOT_GATE port (A: in std_logic; Y: out std_logic); end component;</pre>	<pre>library ieee; use ieee.std_logic_1164.all; entity all_gates is port(A: in std_logic; B: in std_logic; Y_AND: out std_logic; Y_OR: out std_logic; Y_NOT_A: out std_logic; Y_NAND: out std_logic; Y_NOR: out std_logic; Y_XOR: out std_logic; Y_XNOR: out std_logic); end all_gates; architecture dataflow of all_gates is begin Y_AND <= A and B; Y_OR <= A or B; Y_NOT_A <= not A; Y_NAND <= A nand B; Y_NOR <= A nor B; Y_XOR <= A xor B; Y_XNOR <= A xnor B; end dataflow;</pre>	<pre>library IEEE; use IEEE.STD_LOGIC_1164.ALL; entity all_gates is port(A: in std_logic; B: in std_logic; Y_AND: out std_logic; Y_OR: out std_logic; Y_NOT_A: out std_logic; Y_NAND: out std_logic; Y_NOR: out std_logic; Y_XOR: out std_logic; Y_XNOR: out std_logic); end all_gates; architecture behavioral of all_gates is begin process(A, B) begin Y_AND <= A and B; Y_OR <= A or B; Y_NOT_A <= not A; Y_NAND <= A nand B; Y_NOR <= A nor B; Y_XOR <= A xor B; Y_XNOR <= A xnor B; end process; end behavioral;</pre>



```
component NAND_GATE
  port (A, B: in std_logic; Y: out
std_logic);
end component;

component NOR_GATE
  port (A, B: in std_logic; Y: out
std_logic);
end component;

component XOR_GATE
  port (A, B: in std_logic; Y: out
std_logic);
end component;

component XNOR_GATE
  port (A, B: in std_logic; Y: out
std_logic);
end component;

begin
  -- Instantiate the components
  u1: AND_GATE port map(A => A, B
=> B, Y => Y_AND);
  u2: OR_GATE port map(A => A, B
=> B, Y => Y_OR);
  u3: NOT_GATE port map(A => A, Y
=> Y_NOT_A);
  u4: NAND_GATE port map(A => A,
B => B, Y => Y_NAND);
  u5: NOR_GATE port map(A => A, B
=> B, Y => Y_NOR);
  u6: XOR_GATE port map(A => A, B
=> B, Y => Y_XOR);
  u7: XNOR_GATE port map(A => A,
B => B, Y => Y_XNOR);

end structural;

-- AND Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity AND_GATE is
  port (A, B: in std_logic;
        Y: out std_logic);
end AND_GATE;

architecture dataflow of AND_GATE is
begin
  Y <= A and B;
end dataflow;

-- OR Gate Component
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;

entity OR_GATE is
    port (A, B: in std_logic;
          Y: out std_logic);
end OR_GATE;

architecture dataflow of OR_GATE is
begin
    Y <= A or B;
end dataflow;

-- NOT Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NOT_GATE is
    port (A: in std_logic;
          Y: out std_logic);
end NOT_GATE;

architecture dataflow of NOT_GATE is
begin
    Y <= not A;
end dataflow;

-- NAND Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NAND_GATE is
    port (A, B: in std_logic;
          Y: out std_logic);
end NAND_GATE;

architecture dataflow of NAND_GATE
is
begin
    Y <= A nand B;
end dataflow;

-- NOR Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NOR_GATE is
    port (A, B: in std_logic;
          Y: out std_logic);
end NOR_GATE;

architecture dataflow of NOR_GATE is
begin
    Y <= A nor B;
end dataflow;

```

```
-- XOR Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity XOR_GATE is
    port (A, B: in std_logic;
          Y: out std_logic);
end XOR_GATE;


architecture dataflow of XOR_GATE is
begin
    Y <= A xor B;
end dataflow;

-- XNOR Gate Component
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity XNOR_GATE is
    port (A, B: in std_logic;
          Y: out std_logic);
end XNOR_GATE;

architecture dataflow of XNOR_GATE
is
begin
    Y <= A xnor B;
end dataflow;
```

 II.2 LAB EXPERIMENT 2 : WRITE VHDL CODE TO IMPLEMENT THE HALF ADDER CIRCUIT IN FPGA KIT:



Truth Table

A	B	Sum (S)	Carry (Cout)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Top module

```
library ieee;
use ieee.std_logic_1164.all;

entity lab4_ex2 is
    port (SW: in std_logic_vector(17 downto 0);
```

```

        LEDR: out std_logic_vector(17 downto 0);
        LEDG: out std_logic_vector(7 downto 0));
end lab4_ex2;

architecture structure of lab4_ex2 is
    component half_adder
        port(a,b: in std_logic;
             s,c: out std_logic);
    end component;
begin
    LEDR <= SW;
    DUT: half_adder port map(SW(1),SW(0),LEDR(1),LEDR(0));
end structure;


```

Structural	Dataflow	Behavior
<pre> library ieee; use ieee.std_logic_1164.all; entity half_adder is port(a,b: in std_logic; s,c: out std_logic); end half_adder; architecture structural of half_adder is component and_gate port(a,b: in std_logic; y: out std_logic); end component; component xor_gate port(a,b: in std_logic; y: out std_logic); end component; begin u1: and_gate port map(a => a,b=>b,y=>c); u2: xor_gate port map(a =>a,b=>b,y=>s); end structural; library IEEE; use IEEE.STD_LOGIC_1164.ALL; entity and_gate is port (a, b: in std_logic; y: out std_logic); end and_gate; architecture dataflow of and_gate is begin y <= a and b; end dataflow; library IEEE; use IEEE.STD_LOGIC_1164.ALL; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity half_adder is port(a,b: in std_logic; s,c: out std_logic); end half_adder; architecture dataflow of half_adder is begin s <= a xor b; c <= a and b; end dataflow; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity half_adder is port(a,b: in std_logic; s,c: out std_logic); end half_adder; architecture behavior of half_adder is begin process(a,b) begin s <= a xor b; c <= a and b; end process; end behavior; </pre>

```
entity xor_gate is
  port (a, b: in std_logic;
        y: out std_logic);
end xor_gate;

architecture dataflow of xor_gate is
begin
  y <= a xor b;
end dataflow;
```

 II.3 EXPERIMENT 3: WRITE VHDL CODE TO SIMULATE AND IMPLEMENT THE FULL ADDER CIRCUIT IN FPGA KIT:



Inputs			Outputs	
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Top module

```
library ieee;
use ieee.std_logic_1164.all;

entity lab4_ex3 is
  port (
    SW : in std_logic_vector(15 downto 0);
    LEDR : out std_logic_vector(15 downto 0);
    LEDG : out std_logic_vector(7 downto 0)
  );
end lab4_ex3;

architecture structural of lab4_ex3 is
  component full_adder is
    port (
      a, b, cin : in std_logic;
      sum, carry : out std_logic
    );
  end component;

begin
  LEDR <= SW;
  DUT: full_adder port map (SW(2), SW(1), SW(0), LEDG(1), LEDG(0));
end structural;
```

Structural	Dataflow	Behavior
library ieee; use ieee.std_logic_1164.all;	library ieee; use ieee.std_logic_1164.all;	library ieee; use ieee.std_logic_1164.all;

<pre> entity full_adder is port (a, b, cin : in std_logic; sum, carry : out std_logic); end full_adder; architecture structural of full_adder is signal x, y, z : std_logic; component and_gate port (a, b : in std_logic; y : out std_logic); end component; component or_gate port (a, b : in std_logic; y : out std_logic); end component; component xor_gate port (a, b : in std_logic; y : out std_logic); end component; begin x1: xor_gate port map (a => a, b => b, y => x); x2: xor_gate port map (a => x, b => cin, y => sum); a1: and_gate port map (a => x, b => cin, y => y); a2: and_gate port map (a => a, b => b, y => z); a3: or_gate port map (a => y, b => z, y => carry); end structural; library ieee; use ieee.std_logic_1164.all; entity and_gate is port (a, b : in std_logic; y : out std_logic); end and_gate; architecture dataflow of and_gate is begin y <= a and b; end dataflow; library ieee; use ieee.std_logic_1164.all; </pre>	<pre> entity full_adder is port (a, b, cin : in std_logic; sum, carry : out std_logic); end full_adder; architecture dataflow of full_adder is begin sum <= (a xor b) xor cin; carry <= (a and b) or ((a xor b) and cin); end dataflow; </pre>	<pre> entity full_adder is port (a, b, cin : in std_logic; sum, carry : out std_logic); end full_adder; architecture behavior of full_adder is begin process(a,b) begin sum <= (a xor b) xor cin; carry <= (a and b) or ((a xor b) and cin); end process; end behavior; </pre>
---	--	--


```
entity or_gate is
    port (a, b : in std_logic; y : out
std_logic);
end or_gate;


architecture dataflow of or_gate is
begin
    y <= a or b;
end dataflow;

library ieee;
use ieee.std_logic_1164.all;

entity xor_gate is
    port (a, b : in std_logic; y : out
std_logic);
end xor_gate;

architecture dataflow of xor_gate is
begin
    y <= a xor b;
end dataflow;
```

 II.4 EXPERIMENT 4 :WRITE VHDL CODE TO IMPLEMENT 2:1 MULTIPLEXER CIRCUIT IN FPGA KIT :



Truth Table

sel	y
0	i_0
1	i_1

Top module

```
library ieee;
use ieee.std_logic_1164.all;
entity lab4_ex4 is
    port (SW          : in std_logic_vector(17 downto 0);
          LEDR        : out std_logic_vector(17 downto 0);
          LEDG        : out std_logic_vector(7 downto 0));
end lab4_ex4;
```

```
architecture structural of lab4_ex4 is
    component mux21
        port(i: in std_logic_vector(1 downto 0);
              sel: in std_logic;
              y: out std_logic);
    end component;

    begin
        LEDR <= SW;
        DUT: mux21 port map(SW(1 downto 0),SW(2),LEDG(7));
    end structural;
```

Code

```
library ieee;
use ieee.std_logic_1164.all;
entity mux21 is
    port(i: in std_logic_vector(1 downto 0);
          sel: in std_logic;
          y: out std_logic
    );
end mux21;

architecture structural of mux21 is
    signal x: std_logic_vector(3 downto 0);
    component and_gate
        port(a,b: in std_logic;
              y:out std_logic );
    end component;

    component or_gate
        port(a,b: in std_logic;
              y:out std_logic );
    end component;

    component intervert
        port(a: in std_logic;
              y: out std_logic);
    end component;

    begin
        -- Implement the 2-to-1 multiplexer logic
        g1: intervert port map(a => sel, y => x(0));
        g2: and_gate port map(a => i(0), b => x(0), y => x(1));
        g3: and_gate port map(a => i(1), b => sel, y => x(2));
        g4: or_gate port map(a => x(1), b => x(2), y => x(3));

        -- Connect z to output y
        y <= x(3);
    end structural;

    library ieee;
    use ieee.std_logic_1164.all;
    entity and_gate is
        port(    a: in std_logic;
                b: in std_logic;
```

```



        y: out std_logic
    );
end and_gate;

architecture dataflow of and_gate is
begin
    y <= a and b;
end dataflow;

library ieee;
use ieee.std_logic_1164.all;
entity or_gate is
port(    a: in std_logic;
        b: in std_logic;
        y: out std_logic
    );
end or_gate;
architecture dataflow of or_gate is
begin
    y <= a or b;
end dataflow;

library ieee;
use ieee.std_logic_1164.all;
entity intervert is
port(    a: in std_logic;
        y: out std_logic
    );
end intervert;
architecture dataflow of intervert is
begin
    y <= not a;
end dataflow;
    
```

  II.5 EXPERIMENT 5 : WRITE VHDL CODES TO IMPLEMENT 4:1 MULTIPLEXER CIRCUIT IN FPGA KIT:



Truth Table

sel[0]	sel[1]	y
0	0	i ₀
0	1	i ₁
1	0	i ₂
1	1	i ₃

Top module

```
library ieee;
```

```

use ieee.std_logic_1164.all;
entity lab4_ex5 is
    port (SW      : in std_logic_vector(17 downto 0);
          LEDR    : out std_logic_vector(17 downto 0);
          LEDG    : out std_logic_vector(7 downto 0));
end lab4_ex5;

architecture structural of lab4_ex5 is
    component mux41
        port(i: in std_logic_vector(3 downto 0);
              sel: in std_logic_vector(1 downto 0);
              y: out std_logic);
    end component;

    begin
        LEDR <= SW;
        DUT: mux41 port map(SW(3 downto 0),SW(5 downto 4),LEDG(7));
    end structural;

```

Code

```

library ieee;
use ieee.std_logic_1164.all;
entity mux41 is
    port(i: in std_logic_vector(3 downto 0);
          sel: in std_logic_vector(1 downto 0);
          y: out std_logic);
end mux41;

architecture structural of mux41 is
    signal n_s: std_logic_vector(1 downto 0);
    signal x: std_logic_vector(3 downto 0);
    component and_gate
        port (a,b,c: in std_logic;
              y:out std_logic);
    end component;

    component or_gate
        port (a,b,c,d: in std_logic;
              y:out std_logic);
    end component;

    component not_gate
        port (a: in std_logic;
              y:out std_logic);
    end component;
    begin
        g1: not_gate port map(a=>sel(0), y=>n_s(0));
        g2: not_gate port map(a=>sel(1), y=>n_s(1));

        g3: and_gate port map(a=>sel(1),b=>sel(0),c=>i(3),y=>x(3));
        g4: and_gate port map(a=>sel(1),b=>n_s(0),c=>i(2),y=>x(2));
        g5: and_gate port map(a=>n_s(1),b=>sel(0),c=>i(1),y=>x(1));
        g6: and_gate port map(a=>n_s(1),b=>n_s(0),c=>i(0),y=>x(0));

        g7: or_gate port map(a=>x(3),b=>x(2),c=>x(1),d=>x(0),y=>y);
    end structural;

```

```
end structural;

library ieee;
use ieee.std_logic_1164.all;
entity and_gate is
    port (a,b,c: in std_logic;
          y:out std_logic);
end and_gate;

architecture dataflow of and_gate is
    begin
        y <= a and b and c;
    end dataflow;



library ieee;
use ieee.std_logic_1164.all;
entity or_gate is
    port (a,b,c,d: in std_logic;
          y:out std_logic);
end or_gate;

architecture dataflow of or_gate is
    begin
        y <= a or b or c or d;
    end dataflow;

library ieee;
use ieee.std_logic_1164.all;
entity not_gate is
    port (a: in std_logic;
          y:out std_logic);
end not_gate;

architecture dataflow of not_gate is
    begin
        y <= not a;
    end dataflow;
```

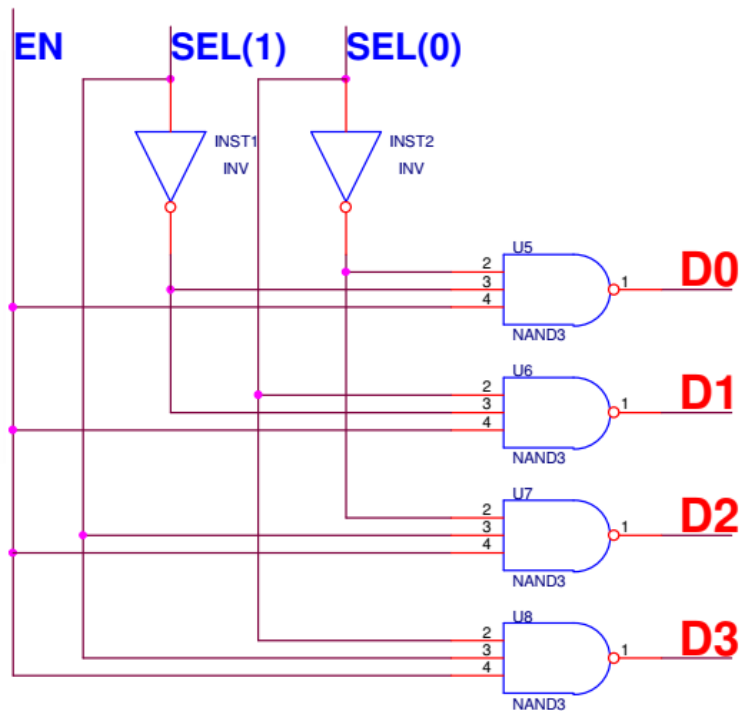 II.6 EXPERIMENT 6 : WRITE VHDL CODE TO IMPLEMENT 2 to 4 DECODER CIRCUIT IN FPGA KIT:



Logic Diagram of 2:4 Decoder

EN	Inputs		Output
	Sel(1)	Sel(0)	D
1	X	X	0
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3

Truth table

Top module

```

library ieee;
use ieee.std_logic_1164.all;
entity lab4_ex6 is
    port (SW      : in std_logic_vector(17 downto 0);
          LEDR    : out std_logic_vector(17 downto 0);
          LEDG    : out std_logic_vector(7 downto 0));
end lab4_ex6;

architecture structural of lab4_ex6 is
    component dec24
        port(en: in std_logic;
              sel: in std_logic_vector(1 downto 0);
              d: out std_logic_vector(3 downto 0));
    end component;

    begin
        LEDR <= SW;
        DUT: dec24 port map(SW(2),SW(1 downto 0),LEDG(7 downto 4));
    end structural;
    
```

Code

```

library ieee;
use ieee.std_logic_1164.all;
entity dec24 is
    port(en: in std_logic;
          sel: in std_logic_vector(1 downto 0);
          d: out std_logic_vector(3 downto 0));
end dec24;

architecture behavioral of dec24 is
begin
    process(en, sel)
    begin
        if (en = '0') then
            d <= "0000";
        else
            case sel is
                when "00" => d <= "0001";
                when "01" => d <= "0010";
                when "10" => d <= "0100";
                when "11" => d <= "1000";
                when others => d <= "0000";
            end case;
        end if;
    end process;
end behavioral;

```

II.7 EXPERIMENT 7 : WRITE VHDL CODE TO IMPLEMENT 8 TO 3 ENCODER WITH PRIORITY CIRCUIT IN FPGA KIT:

Truth table for 8-input priority encoder

EN	DIN (7:0)	EOUT
0	X X X X X X X X	0
1	X X X X X X X 0	0
1	X X X X X X 0 1	1
1	X X X X X 0 1 1	2
1	X X X X 0 1 1 1	3
1	X X X 0 1 1 1 1	4
1	X X 0 1 1 1 1 1	5
1	X 0 1 1 1 1 1 1	6
1	0 1 1 1 1 1 1 1	7
1	1 1 1 1 1 1 1 1	0

Top module

```

library ieee;
use ieee.std_logic_1164.all;

```

```
entity lab4_ex7 is
    port (SW      : in std_logic_vector(17 downto 0);
          LEDR    : out std_logic_vector(17 downto 0);
          LEDG    : out std_logic_vector(7 downto 0));
end lab4_ex7;

architecture structural of lab4_ex7 is
    component enc83
        port(en: in std_logic;
              d: in std_logic_vector(7 downto 0);
              y: out std_logic_vector(2 downto 0));
    end component;


    begin
        LEDR <= SW;
        DUT: enc83 port map(SW(8),SW(7 downto 0),LEDG(7 downto 5));
    end structural;
```

Code

```
library ieee;
use ieee.std_logic_1164.all;
entity enc83 is
    port(en: in std_logic;
          d: in std_logic_vector(7 downto 0);
          y: out std_logic_vector(2 downto 0));
end enc83;

architecture behavioral of enc83 is
begin
    process(en, d)
    begin
        if (en = '0') then
            y <= "000";
        else
            case d is
                when "00000001" => y <= "000";
                when "00000011" => y <= "001";
                when "00000111" => y <= "010";
                when "00001111" => y <= "011";
                when "00011111" => y <= "100";
                when "00111111" => y <= "101";
                when "01111111" => y <= "110";
                when "11111111" => y <= "111";
                when others => y <= "000";
            end case;
        end if;
    end process;
end behavioral;
```

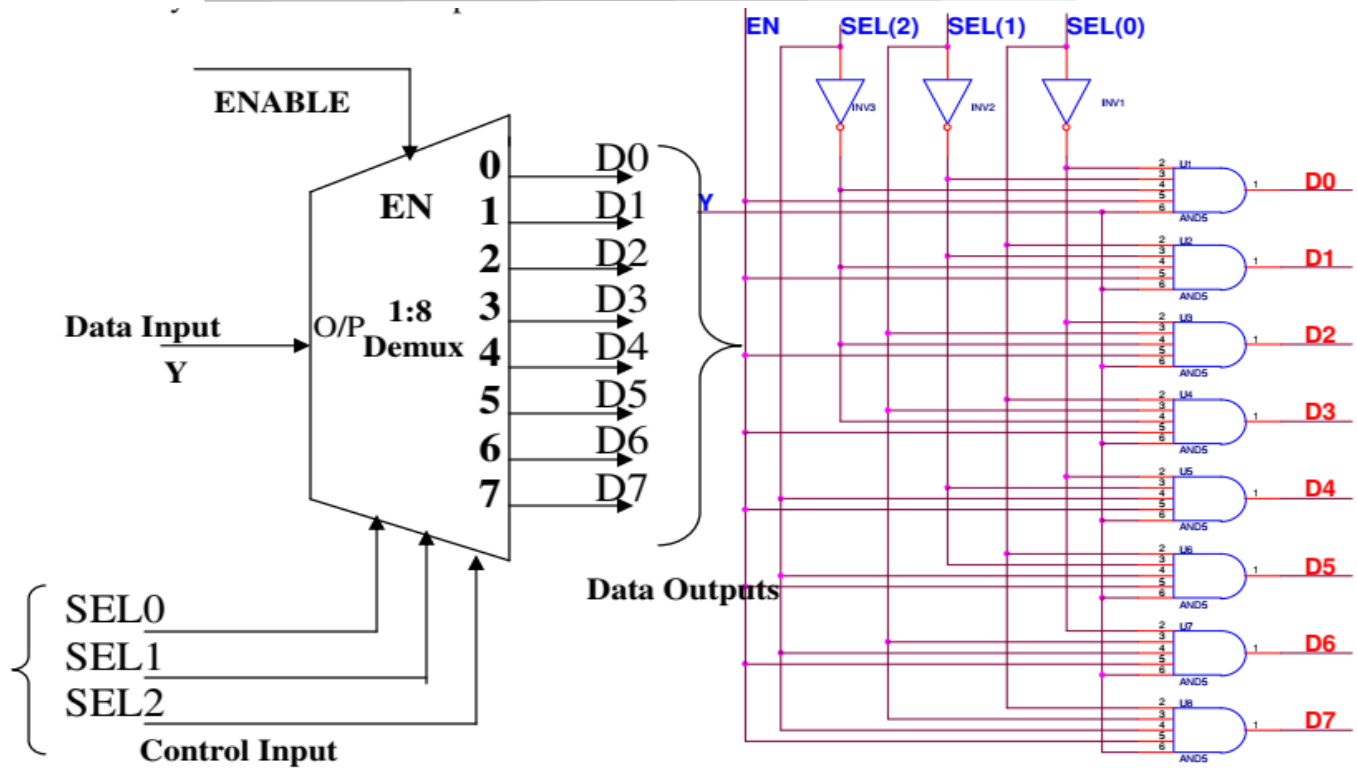II.8 EXPERIMENT 8 : WRITE VHDL CODES TO IMPLEMENT 1 TO 8 DEMULTIPLEXER CIRCUIT IN FPGA KIT:



Block Diagram of 1:8 Demux

Logic Diagram

Truth Table

EN	CONTROL INPUTS			OUTPUTS
	SEL(3)	SEL(3)	SEL(3)	
0	X	X	X	0
1	0	0	0	D0=Y
1	0	0	1	D1=Y
1	0	1	0	D2=Y
1	0	1	1	D3=Y
1	1	0	0	D4=Y
1	1	0	1	D5=Y
1	1	1	0	D6=Y
1	1	1	1	D7=Y

Top module

```

library ieee;
use ieee.std_logic_1164.all;
entity lab4_ex8 is
    port (SW          : in std_logic_vector(17 downto 0);
          LEDR       : out std_logic_vector(17 downto 0);
          LEDG       : out std_logic_vector(7 downto 0));
end lab4_ex8;

```

```
architecture structural of lab4_ex8 is
  component demux18
    port(i: in std_logic;
          en: in std_logic;
          sel: in std_logic_vector(2 downto 0);
          d: out std_logic_vector(7 downto 0));
  end component;

  begin
    LEDR <= SW;
    DUT: demux18 port map(SW(4),SW(3),SW(2 downto 0),LEDG(7 downto 0));
  end structural;
```

Code

```
library ieee;
use ieee.std_logic_1164.all;
entity demux18 is
  port(i: in std_logic;
        en: in std_logic;
        sel: in std_logic_vector(2 downto 0);
        d: out std_logic_vector(7 downto 0));
end demux18;

architecture structural of demux18 is
  signal n_s: std_logic_vector(2 downto 0);
  component not_gate
    port(a: in std_logic;
          y: out std_logic);
  end component;

  component and_gate
    port(a,b,c,d,e: in std_logic;
          y: out std_logic);
  end component;

  begin
    g1: not_gate port map(a=>sel(0), y=>n_s(0));
    g2: not_gate port map(a=>sel(1), y=>n_s(1));
    g3: not_gate port map(a=>sel(2), y=>n_s(2));

    g4: and_gate port map(a=>n_s(0), b=>n_s(1), c=>n_s(2),d=>en,e=>i, y=>d(0));
    g5: and_gate port map(a=>sel(0), b=>n_s(1), c=>n_s(2),d=>en,e=>i, y=>d(1));
    g6: and_gate port map(a=>n_s(0), b=>sel(1), c=>n_s(2),d=>en,e=>i, y=>d(2));
    g7: and_gate port map(a=>sel(0), b=>sel(1), c=>n_s(2),d=>en,e=>i, y=>d(3));
    g8: and_gate port map(a=>n_s(0), b=>n_s(1), c=>sel(2),d=>en,e=>i, y=>d(4));
    g9: and_gate port map(a=>sel(0), b=>n_s(1), c=>sel(2),d=>en,e=>i, y=>d(5));
    g10: and_gate port map(a=>n_s(0), b=>sel(1), c=>sel(2),d=>en,e=>i, y=>d(6));
    g11: and_gate port map(a=>sel(0), b=>sel(1), c=>sel(2),d=>en,e=>i, y=>d(7));
  end structural;

library ieee;
use ieee.std_logic_1164.all;
entity and_gate is
```



```
port(  a: in std_logic;
      b: in std_logic;
      c: in std_logic;
      d: in std_logic;
      e: in std_logic;
      y: out std_logic
);
end and_gate;

architecture dataflow of and_gate is
begin
  y <= a and b and c and d and e;
end dataflow;

library ieee;
use ieee.std_logic_1164.all;
entity not_gate is
port(  a: in std_logic;
      y: out std_logic
);
end not_gate;

architecture dataflow of not_gate is
begin
  y <= not a;
end dataflow;
```

II.9 EXPERIMENT 9 : WRITE VHDL CODES TO IMPLEMENT N-BIT COMPARATOR CIRCUIT IN FPGA KIT WITH FOLLOWING VHDL REFERENCED CODE

Top module

```
library ieee;
use ieee.std_logic_1164.all;
entity lab4_ex9 is
generic(n: natural :=4);
  port (SW      : in std_logic_vector(17 downto 0);
        LEDR   : out std_logic_vector(17 downto 0);
        LEDG   : out std_logic_vector(7 downto 0));
end lab4_ex9;

architecture structural of lab4_ex9 is
  component comparator
    port(  A:      in std_logic_vector(n-1 downto 0);
          B:      in std_logic_vector(n-1 downto 0);
          less:    out std_logic;
          equal:   out std_logic;
          greater: out std_logic);
  end component;

begin
  LEDR <= SW;
  DUT: comparator port map(SW(2*n-1 downto n),SW(n-1 downto 0),LEDG(7),LEDG(6),LEDG(5));
end structural;
```

Code

```
library ieee;
use ieee.std_logic_1164.all;

entity comparator is
generic(n: natural :=4);
port(  A:      in std_logic_vector(n-1 downto 0);
      B:      in std_logic_vector(n-1 downto 0);
      less:    out std_logic;
      equal:   out std_logic;
      greater: out std_logic
);
end comparator;
architecture behv of comparator is
begin
  process(A,B)
  begin
    if (A>B) then
      less <= '0';
      equal <= '0';
      greater <= '1';
    elsif (A=B) then
      less <= '0';
      equal <= '1';
      greater <= '0';
    else
      less <= '1';
      equal <= '0';
      greater <= '0';
    end if;
  end process;
end behv;
```

II.10 EXPERIMENT 10 : WRITE VHDL CODES TO IMPLEMENT N-BIT ALU CIRCUIT IN FPGA KIT WITH FOLLOWING VHDL REFERENCED CODE

Top module

```
library ieee;
use ieee.std_logic_1164.all;
entity lab4_ex10 is
generic(N: natural :=4);
  port (SW      : in std_logic_vector(17 downto 0);
        LEDR   : out std_logic_vector(17 downto 0);
        LEDG   : out std_logic_vector(7 downto 0));
end lab4_ex10;

architecture structural of lab4_ex10 is
  component ALU
    port(  A:      in std_logic_vector(N-1 downto 0);
          B:      in std_logic_vector(N-1 downto 0);
          Op:     in std_logic_vector(2 downto 0);
          Res:    out std_logic_vector(N-1 downto 0));
  end component;
```

```
begin
    LEDR <= SW;
    DUT: ALU
        port map(
            SW(2*N-1 downto N),
            SW(N-1 downto 0),
            SW(2*N+2 downto 2*N),
            LEDG(N-1 downto 0));
end structural;
```

Code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity ALU is
generic(N: natural :=4);

port(  A:      in std_logic_vector(N-1 downto 0);
       B:      in std_logic_vector(N-1 downto 0);
       Op:     in std_logic_vector(2 downto 0);
       Res:    out std_logic_vector(N-1 downto 0));
end ALU;

architecture behv of ALU is
begin

    process(A,B,Op)
    begin

        case Op is
            when "000" =>
                Res <= A + B;
            when "001" =>
                Res <= A - B;
            when "010" =>
                Res <= not A ;
            when "011" =>
                Res <= not (A and B);
            when "100" =>
                Res <= not (A or B);
            when "101" =>
                Res <= A and B;
            when "110" =>
                Res <= A or B;
            when "111" =>
                Res <= A xnor B;
        end case;

    end process;

end behv;
```